

LDO Design




Ke-Horng Chen

NCTU ECE

2007 Spring

LOW DROP-OUT REGULATORS

 
- ❑ Low-power-consumption LDO have been developed to increase the lifetime of battery effectively
 - When the LDO is implemented in CMOS technologies, the low-ground-current feature is an advantage to portable applications
 - These circuits operate under lower voltage condition
 - High current efficiency become necessary to maximize the lifetime of the battery



Characteristic

■ Block Level Description –

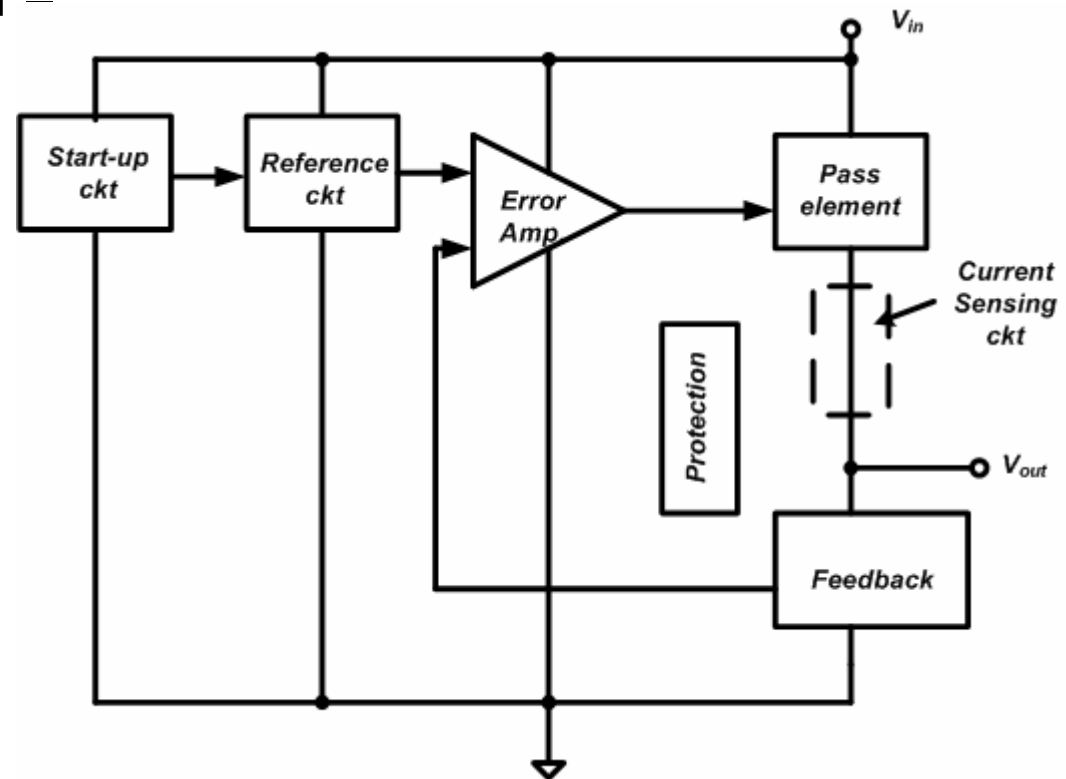- Start-up circuit
- Reference
- Protection circuit
- Current sense element
- Error amplifier (EA)
- Pass element
- Feedback network



Specifications

- ❑ Drop-out voltage
- ❑ Line regulation
- ❑ Load regulation
- ❑ Tolerance over temperature
- ❑ Output voltage variation **resulting from transient load-current step**
- ❑ Output capacitor and ESR range
- ❑ Quiescent current flow
- ❑ Maximum load current
- ❑ Input/output voltage range

$$V_{drop-out} = I_{Load} R_{on}$$

$$Line - regulation = \frac{\Delta V_o}{\Delta V_s}$$

$$Load - regulation = \frac{\Delta V_o}{\Delta I_L} = \frac{R_{o-pass}}{1 + A\beta}$$

$$TC = \frac{1}{V_o} \frac{\partial V_o}{\partial T_{emp}} \approx \frac{1}{V_o} \frac{\Delta V_{TC}}{\Delta T_{emp}}$$

$$= \frac{[\Delta V_{TC,ref} + \Delta V_{TC,V_{os}}] \frac{V_o}{V_{ref}}}{V_o \Delta T_{emp}}$$

$$\Delta V_{tr} = \frac{I_{load-max}}{C_o + C_b} \Delta t + \Delta V_{esr}$$

$$Accuracy_{system} = \frac{V_{o(max)} - V_{o(min)}}{V_o}$$


$$V_{o-min} \leq \Delta V_{LNR} + \Delta V_{LDR} + \Delta V_{TC} + \Delta V_{tr} + V_{reference} \left\langle \frac{V_o}{V_{ref}} \right\rangle \leq V_{o-max}$$

$$V_{reference} = V_{ref} + \Delta V_{TC_{ref}} + \Delta V_{LNR_{ref}} \pm V_{os}$$

System Design Considerations

- ❑ Enhance performance of LDO regulators for battery powered electronic
 - Low quiescent current flow for increase battery life
 - Low voltage operation
 - High output current
- ❑ The intrinsic issues in design :
 - Stability
 - Maximum output current
 - Regulating performance
- ❑ Analysis
 - AC Analysis
 - Transient Analysis

System Model under Loading Conditions

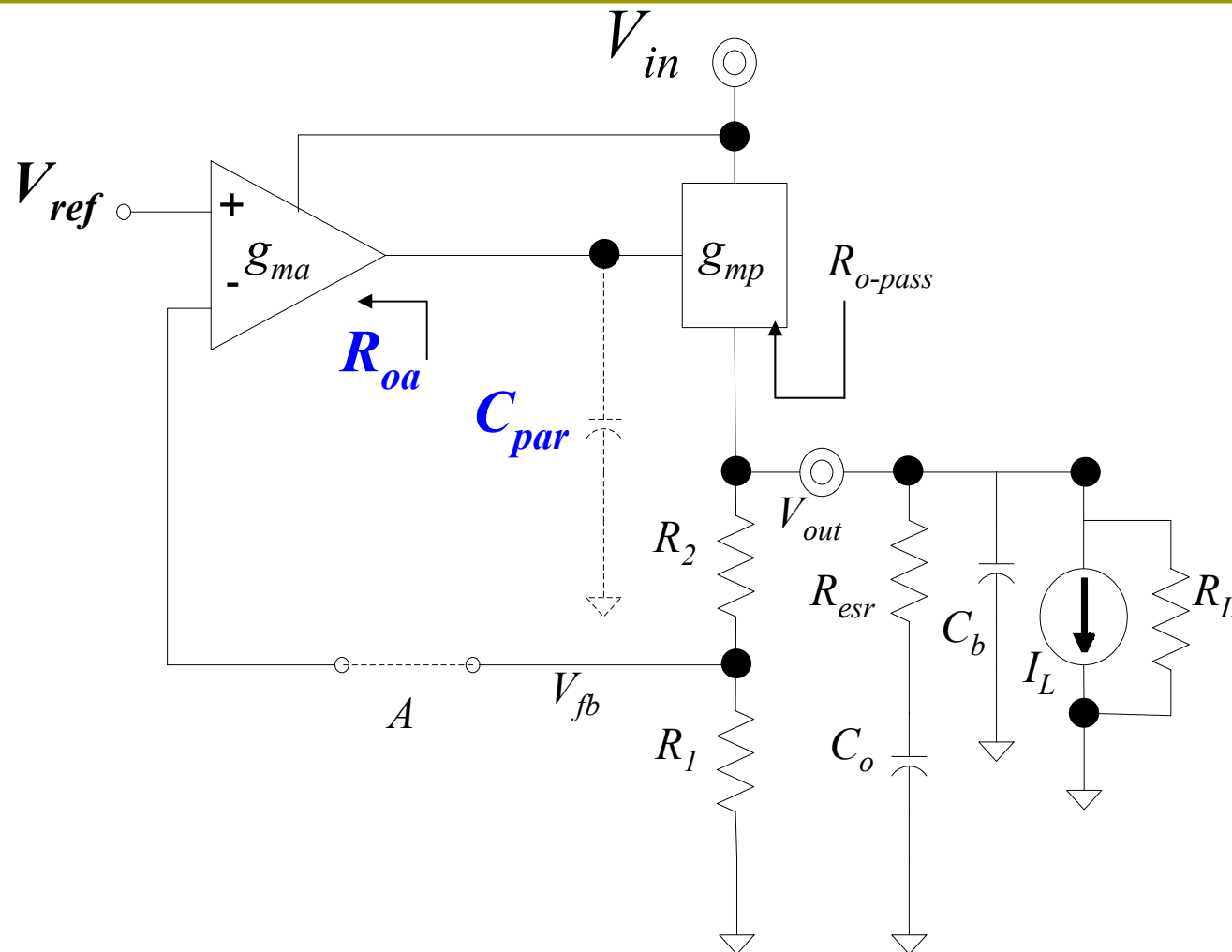

Frequency Response

$$\frac{V_{fb}}{V_{ref}} = |A_v| = \frac{g_{ma} R_{oa} g_{mp} Z}{[1 + s R_{oa} C_{par}]} \times \frac{R_1}{[R_1 + R_2]}$$

$$Z = R_X \parallel \frac{1 + s R_{esr} C_o}{s C_o} \parallel \frac{1}{s C_b}$$

$$= \frac{R_X [1 + s R_{esr} C_o]}{s^2 R_X R_{esr} C_o C_b + s [R_X + R_{esr}] C_o + s R_X C_b + 1}$$

$$R_X = R_{o-pass} \parallel (R_1 + R_2)$$

If $C_o \gg C_b$ (Typical condition)

$$Z \approx \frac{R_X [1 + s R_{esr} C_o]}{[1 + s (R_X + R_{esr}) C_o] \cdot [1 + s (R_X \parallel R_{esr}) C_b]}$$


$R_1 + R_2 \gg R_{o-pass}$ (Especially at high current)

$$\Rightarrow R_X \approx R_{o-pass}$$

- g_{ma} and g_{mp} refer to the transconductance of the amplifier and the pass element respectively
- R_{oa} is the output resistance of the amplifier
- C_{par} refers to the parasitic capacitance introduced by the pass element
- Z is the impedance seen at V_{out}

Frequency Response (cont'd)

- In a conventional LDO, ESR of output capacitor generates this zero to guarantee phase margin better than 45 degrees
- The ESR is not properly specified and varies with temperature
- The high-frequency bypass capacitors placed in parallel with the output capacitor form a pole further decrease the phase margin
- Ceramic capacitors are cheaper than tantalum capacitors, but ESR of ceramic capacitors typically less than $50m\Omega$
- ESR increases the overshoot drastically if large resistors are used

 


Design Challenge

- The worst-case stability condition arises when the phase margin is at its lowest point (UGF goes high)
 - This happens when the load-current is **at its peak value**
- P_1 **increases at a faster rate** than *the gain of the system decrease*
- The **type and value of the output capacitor** determine the location of P_1 , P_2 , and Z_1

$$\uparrow\uparrow P_1 = \frac{1}{2\pi R_{o-pass} C_o} \propto \lambda I_o \propto I_o$$
 
$$\downarrow \text{Gain} = g_{mp} R_{o-pass} \propto \sqrt{I_o} \times \frac{1}{\lambda I_o} \propto \frac{1}{\sqrt{I_o}}$$



Parasitic Pole Requirements

- ❑ The parasitic pole of the system can be identified as P_3 and the internal poles of the error amplifier
 - Requirement : **parasitic pole must be greater than UGF**
 - Ensuring that P_3 is at high frequencies is **an especially difficult task** to undertake *in a low current environment*
- ❑ The pole is defined by
 - The large parasitic capacitance (C_{par}) resulting from a large pass device
 - The output resistance of the amplifier (R_{oa})
- ❑ **Low quiescent current** and **frequency design issues** have **conflicting requirements** that necessitate compromises



Maximum Load Regulation Performance

- Load regulation performance is a function of the **open-loop gain** of the system and can be expressed as:

$$R_o = \frac{\Delta V_{LDR}}{\Delta I_o} = \frac{R_{o-pass}}{1 + A_{ol}\beta}$$

- The regulator yields better load regulation performance as the open-loop gain increases
 - The gain is limited **by the closed-loop bandwidth of the system**
 - The closed-loop bandwidth is equivalent to the open-loop UGF*
 - The **worst-case condition** occurs **when Z_l is at low frequencies and P_2 is at high frequencies**
 - Which corresponds to **the maximum value of ESR** and the **lowest bypass capacitance C_b**

  Typical LDO Transient Response to a Load-current Step



Transient Analysis: Typical response

- The worst-case time (Δt_1) required for the loop to respond is specified by ΔV_{tr-max} , which is a function of C_o , ESR of C_o , C_b , and $I_{Load-max}$

$$\Delta V_{tr-max} \approx \frac{I_{Load-max}}{C_o + C_b} \Delta t_1 + \Delta V_{esr}$$

$$\Delta t_1 \approx \frac{[C_o + C_b]}{I_{Load-max}} [\Delta V_{tr-max} - \Delta V_{esr}]$$

Typical Response (cont'd)

- Δt_1 is not only a function of **bandwidth** but also defined by the **internal slew-rate** associated with the parasitic capacitance C_{par} of the pass element

$$\Delta t_1 \approx \frac{1}{BW_{cl}} + t_{sr} = \frac{1}{BW_{cl}} + C_{par} \frac{\Delta V}{I_{sr}} = 2\mu + 20\mu = 22\mu$$

- Where BW_{cl} is the closed-loop bandwidth of the system, t_{sr} is the slew-rate time associated with C_{par} , ΔV is the voltage variation at C_{par} , and I_{sr} is the slew-rate limited current
- For instance, if BW_{cl} is 500kHz, C_{par} is 200pF, ΔV is 0.5V, I_{sr} is 5 μ A, C_o is 10uF, R_{esr} is 0, and $I_{load-max}$ is 100mA
 - The maximum output voltage variation is approximately 220mV

Typical response (cont'd)

- Once the slew-rate condition is terminated, the output voltage recovers and settles to its final value

$$\Delta V_2 \approx R_{o-reg} I_{Load-max}$$

- R_{o-reg} is the closed-loop output resistance of the regulator

- The settling time (Δt_2) is dependent on
 - The time required for the pass device to fully charge the load capacitors
 - The phase margin of the open-loop frequency response

Transient Analysis


- The **momentary current supplied** by the power device ($I_{Load-max}$ until the circuit **reacts to shut it off**) flows to the output capacitor C_o and the C_b (the current is no longer flowing to the load)
 - Consequently, the capacitors charge up and a temporary voltage drop is created across R_{esr}

$$\Delta V_3 \approx \frac{I_{Load-max}}{C_o + C_b} \Delta t_3 + \Delta V_{esr} \approx \frac{I_{Load-max}}{C_o + C_b} \cdot \left(\frac{1}{BW_{cl}} + t_{sr} \right) + \Delta V_{esr}$$




- When the output transistor is finally shut off (after Δt_3) the variation settles down to ΔV_4 , **the voltage charged on the capacitors** ($\Delta V_4 \approx \Delta V_3 - \Delta V_{esr}$)

$$\Delta t_4 \approx \frac{C_o + C_b}{I_{pull-down}} \Delta V_4 = \frac{[C_o + C_b] R_1}{V_{ref}} \Delta V_4$$

 Amplifier Design Issues



Performance Enhancements


- Enhancing performance **without** incurring significant costs in **quiescent current** or **voltage headroom** benefit the overall design of LDOs
 - Current Efficiency  ■ Quiescent current flow (must be low)
 - Current Boosting  ■ Maximum output current capabilities
 - Load Regulation  ■ Regulation performance

Current Efficiency

- $Efficiency_{current} = \frac{I_{Load}}{I_{Load} + I_q}$
- The limitation of current efficiency of low drop-out regulators are maximum load-current and transient output voltage variation
 - They typically require more I_q for increased performance
- Maximum output current and low input voltage affect the characteristics of the pass element which defines the I_q requirement of the error Amp
- When the maximum load-current specification increases
 - The size of the pass devices ↑
 - The EA's load capacitances ↑
 - Phase-margin ↓ (P_3) ↓
 - The stability *is compromised* unless the output impedance (R_{oa}) of the EA is reduced accordingly → more I_q

Slew-Rate Dependent Boost Circuit

 - Handling an instantaneous load-current stimulus is translated to the slew-rate requirement of driving the pass device
 - Two normally off switches are added around a unity gain buffer constituting the output stage of the amplifier
 - Conduct significant current \Leftrightarrow where a voltage difference across the unity gain buffer develops to be large enough to turn either of the MOS devices on



Adjust the threshold voltage by using a double gate MOS device


- The voltage at the floating gate (V_g), assuming that the source is grounded, is dictated by

$$V_g = \frac{V_1 C_1}{C_{total}} + \frac{V_2 C_2}{C_{total}} \quad [C_{total} \text{ is } C_1 + C_2 + C_g]$$

- V_{th1} is the effective threshold voltage of terminal one and V_{th} is the threshold voltage seen at the floating gate


$$V_{th1} = \frac{V_{th} C_{total}}{C_1} - \frac{V_2 C_2}{C_1}$$

 - If $C_1 = C_2 = 8C_g$, $V_2 = 1.0V$, and $V_{th} = 0.7V$ then
 - Yield a lower effective threshold voltage $V_{th1} = 0.49V$
- **Disadvantage:** generate V_{nbias} and V_{pbias}



Connect to the gate of the pass devices

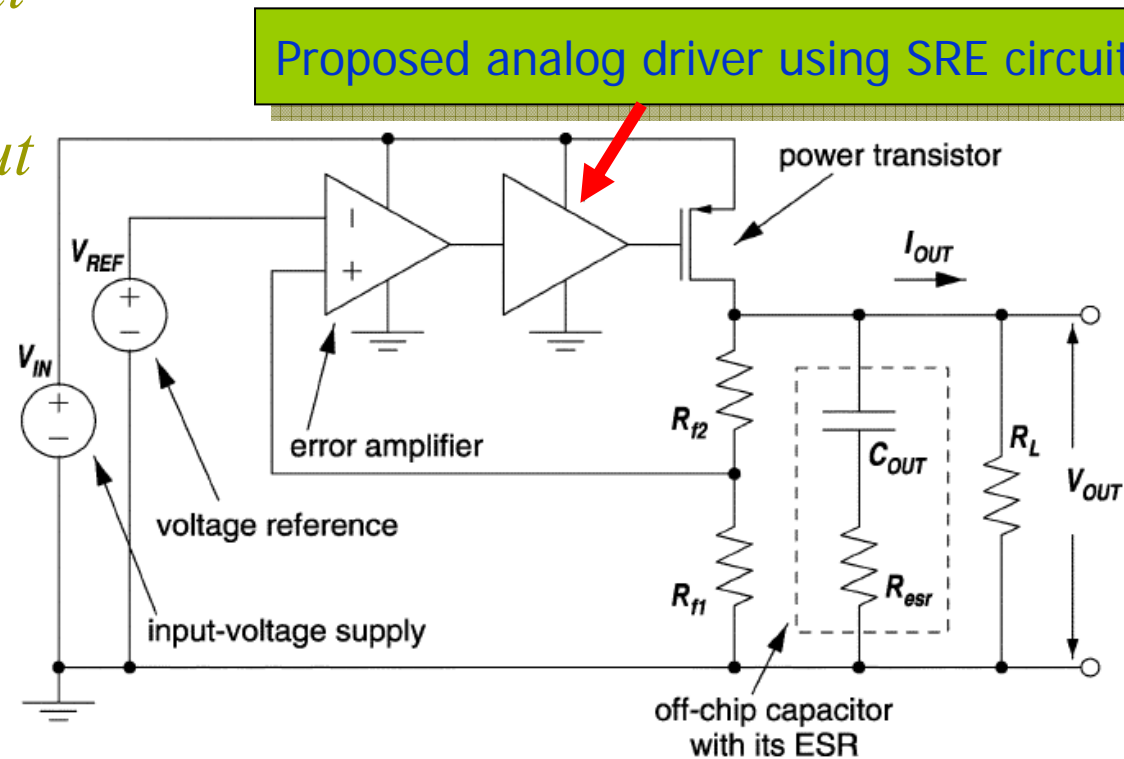Slew-Rate Enhancement Circuits for CMOS Low-Dropout Regulators



□ Design problem


- Large gate capacitance of power transistor degrades the loop-gain bandwidth and slew rate at the gate drive of the LDO

□ Solution


- A voltage buffer/driver can be inserted between the error amp. and the power transistor
- It is difficult to realize a good voltage buffer to meet the requirements

Design considerations of proposed analog driver

■ Proposed block diagram

 


■ Rincon-Mora's proposed

 

- Need low threshold device and forward bulk-biasing

Age Group	Percentage
18-24	15%
25-34	25%
35-44	30%
45-54	20%
55-64	10%
65-74	5%
75-84	2%
85+	1%


Drive circuit

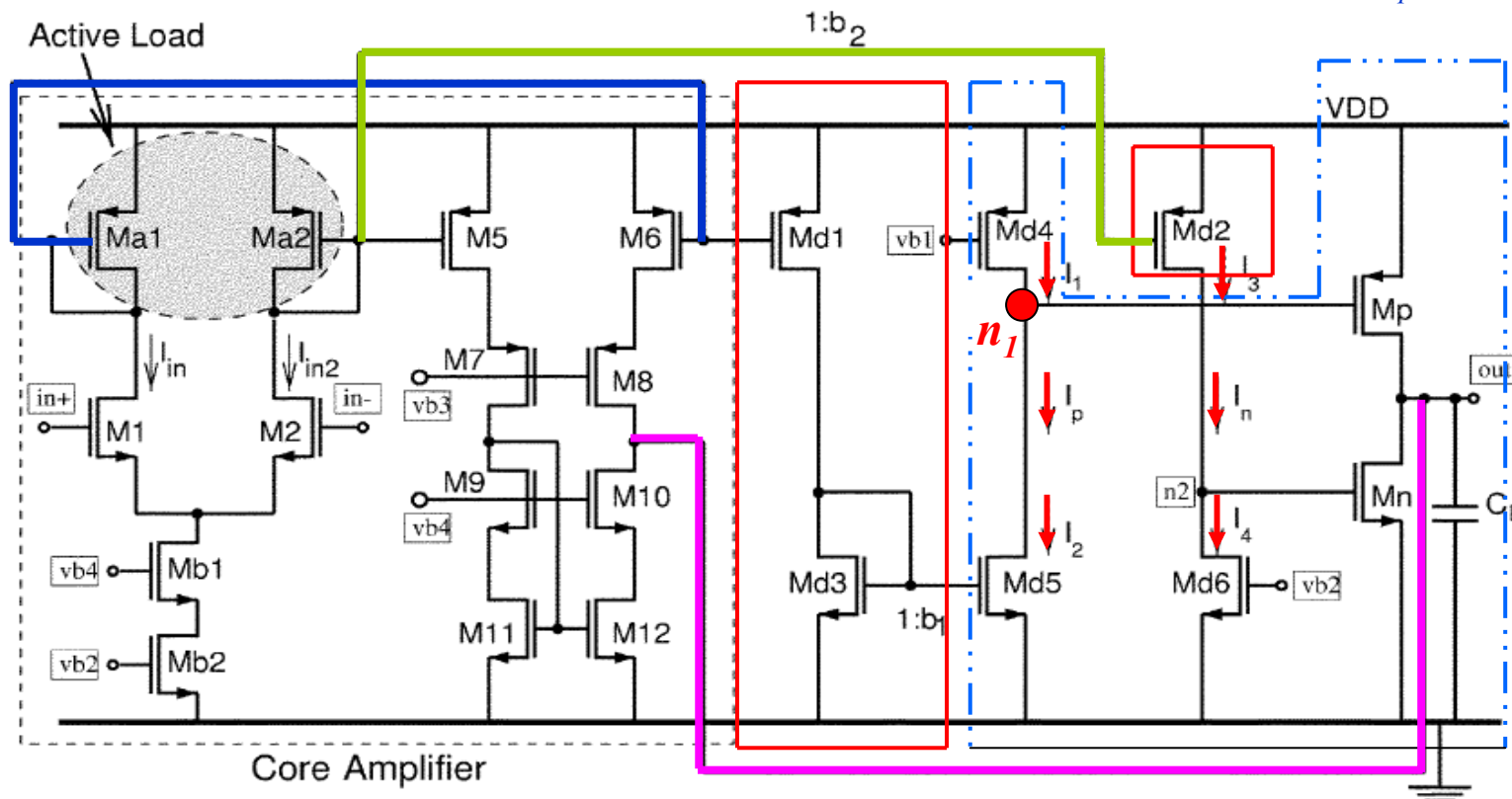

- 24



Simulation result

 - The simulation results of ac responses of the core amplifier **with and without the SRE circuit** driving a load capacitance of $470pF$
 - The SRE circuit **does not affect the ac responses** of the core amplifier




Experiment results

  - It does not have significant transient overshoot even if the load capacitance is changed by more than two times
 - The SRE circuit *is properly shut down before and end of the slewing periods*



■ 470-pF load

 


■ 1-nF load

Experiment results

	Current-Mirror Amp. without SRE*	Current-Mirror Amp. with SRE	
Static Power (mW)	0.22	0.28	27.3%
Gain@10Hz	74 dB	73 dB	
GBW	56 kHz	57 kHz	
Phase Margin	89.7°	90°	
SR+/SR- (V/μs)	0.037/0.0368 (C _L =470pF) 0.017/0.017 (C _L =1nF)	1.5/1.73 (C _L =470pF) 0.7/0.81 (C _L =1nF)	43X
Ts+/Ts- (1%) (μs)	31.3/31.4 (C _L =470pF) 66.7/66.7 (C _L =1nF)	0.79/0.61 (C _L =470pF) 1.44/1.09 (C _L =1nF)	44X
Area (mm ²)	N.A.	0.027	
Supply Voltage	3 V		
Loading capacitor	1 MΩ // 470 pF		


Experiment results

 - The load transient response of the LDO is improved by 2.3 times with 50mA output-current change



Current Efficient Buffer

- The increase in current in the buffer stage aids the circuit
 - By pushing the parasitic pole at its output (P_3) to **higher frequencies**
 - And by increasing the current available for **slew-rate conditions**
- Thus, the biasing conditions for the case of **zero load-current** can be designed to **utilize a minimum amount of current**
 - Which yields maximum current efficiency and prolonged battery life

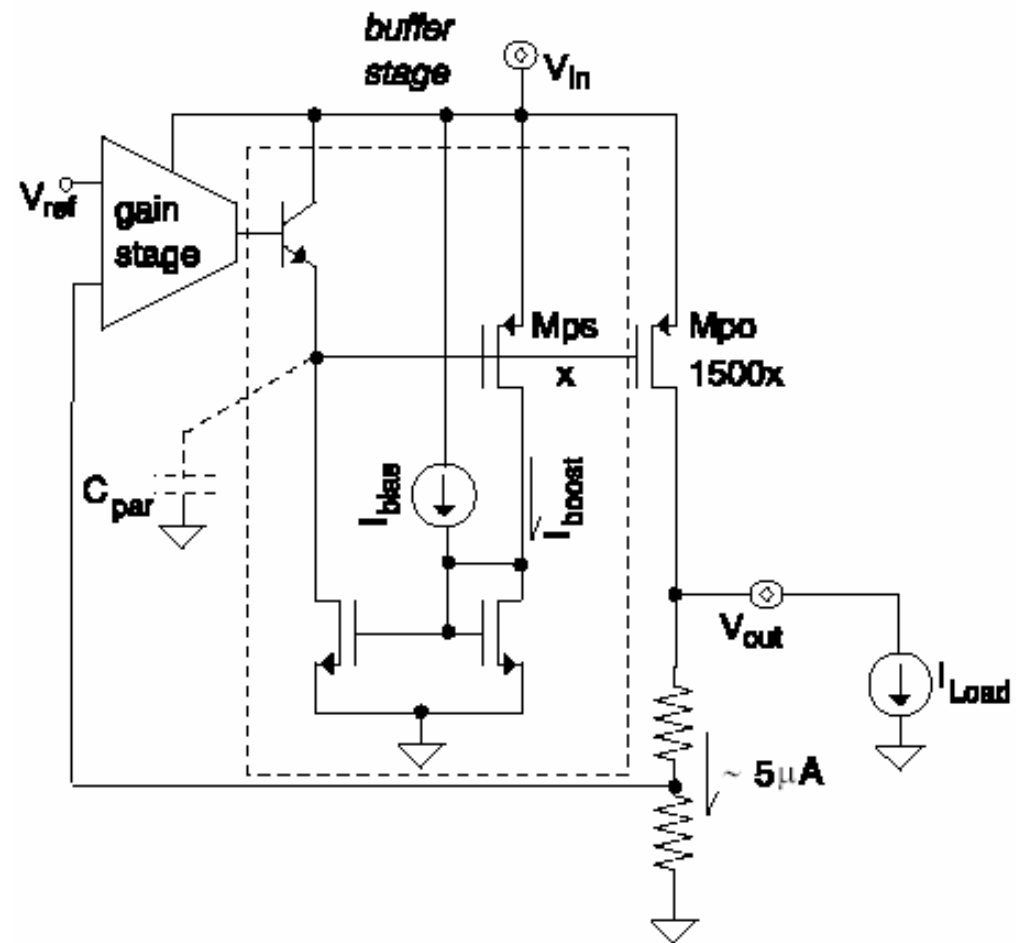

Frequency Response

- Low load current :


$$P_1 \approx \frac{1}{2\pi R_{o-pass} C_o} \approx \frac{\lambda I_{Load}}{2\pi C_o}$$

$$P_{3no-load-current} \approx \frac{g_{mnpn}}{2\pi C_{par}} = \frac{I_{bias}}{2\pi V_t C_{par}} \geq UGF_{min}$$

- High load current : ??

$$A_v \approx A_{amp} g_{mp} R_{o-pass} \propto \frac{\sqrt{I_{Load}}}{I_{Load}} = \frac{1}{\sqrt{I_{Load}}}$$

Frequency Response

 

Frequency Response

- As I_{Load} increases, $P_1 \uparrow \uparrow$ (UGF $\uparrow \uparrow$) faster than $A_v \downarrow$
 $\rightarrow P_3$ is also required to increase with I_{Load} , which is achieved by the load dependent boost current

- Load dependent boost current :

$$P_3 \approx \frac{g_{mnpn}}{2\pi C_{par}} = \frac{I_{bias} + I_{boost}}{2\pi V_t C_{par}} \approx \frac{I_{bias} + kI_{Load}}{2\pi V_t C_{par}}$$

- As $I_{Load} \uparrow$, design P_3 increases at a faster rate than the UGF

$$P_{3-rate} = \frac{\partial P_3}{\partial I_{Load}} \approx \frac{k}{2\pi V_t C_{par}} \geq P_{1-rate} \approx \frac{\lambda}{2\pi C_o} > UGF_{rate} \Rightarrow k \geq \frac{\lambda V_t C_{par}}{C_o}$$

- Where P_{3-rate} , P_{1-rate} and UGF_{rate} are the rates with respect to load-current of pole P_3 , pole P_1 , and the unity gain frequency respectively

Transient Response

- During a load-current transition from zero to maximum value :

$$\Delta t_1 \approx t_{amp} + t_{Mpo} + t_{Mps-on} + t_{latch-up}$$

$$\approx \frac{1}{BW_{cl}} + t_{Mps-on} + t_{latch-up} \left[\text{where } \frac{1}{BW_{cl}} \approx t_{amp} + t_{Mpo} \right]$$


- The composite buffer stage
 - A localized positive feedback circuit
 - The positive feedback gain is *less than one*
 - Attempts to latch up until the output transistor is fully turned on
 - At which point , the error amplifier forces the circuit back into the linear region

An Example

- $C_{par}=200pF$, the voltage change required for the output PMOS transistor (ΔV_{sg}) is 0.5V, the closed-loop bandwidth of the system is 1MHz, and the response time (Δt_l) is confined to be less than 5us
 - The slew-rate current ($I_{sr}=I_{bias}$) required for a class A buffer is approximately 25uA
 - For the case of "current efficient-transient boost LDO buffer stage", a dc current bias (I_{bias}) of only 1uA can provide the same performance

Transient Response

 - The output voltage variation is decreased as a result of a reduction in response time
- Does not come at the expense of additional quiescent current flow during zero-load-current conditions
- Achieve maximum current efficiency and battery life




Maximum Output Current

- The two main limitations of low voltage operation lie in the output current capabilities of the pass device (power switch) and voltage headroom
- The threshold voltage decreased as V_{sb} increases thereby effectively increasing the gate drive of the power PMOS transistor (pass device)

$$I_{sd} \approx \frac{K_p W}{2L} [V_{sg} - V_{th}]^2$$
$$\approx \frac{K_p W}{2L} \left\langle V_{sg} - |V_{t0}| - \gamma \left[\sqrt{2|\phi_f| - V_{sb}} - \sqrt{2|\phi_f|} \right] \right\rangle^2$$

Current Boosting

 - The ability to shut off M_{po} is not degraded since the forward bias voltage is a function of load-current
 - At low load-currents I_{boost} is low and V_{sb} is close to zero
 - At high load-current, I_{boost} and V_{sb} increase thereby decreasing the threshold voltage and increasing the effective gate drive of the output PMOS device



Drop-out Voltage

- The method of forward biasing the source to bulk junction also yields lower drop-out voltages
 - The on resistance of the pass device (M_{po}) is reduced
 - When the regulator is in drop-out, M_{po} is characteristically in the triode region and exhibits the well known current relationship

$$I_{sd} \approx \frac{K_p W}{2L} \left\langle [V_{sg} - V_{th}] V_{sd} - V_{sd}^2 \right\rangle \approx \frac{K_p W}{2L} [V_{sg} - V_{th}] V_{sd}$$


$$\downarrow R_{on} \approx \frac{V_{sd}}{I_{sd}} \approx \frac{2L}{K_p W} \cdot \frac{1}{[V_{sg} - V_{th}]} \approx \frac{2L}{K_p W} \cdot \frac{1}{\left\langle V_{sg} - |V_{t0}| - \gamma \left[\sqrt{2|\phi_f| - V_{sb}} - \sqrt{2|\phi_f|} \right] \right\rangle}$$

$$\downarrow V_{do} \approx R_{on} I_{Load} \approx \frac{2L}{K_p W} \cdot \frac{I_{Load}}{\left\langle V_{sg} - |V_{t0}| - \gamma \left[\sqrt{2|\phi_f| - V_{sb}} - \sqrt{2|\phi_f|} \right] \right\rangle}$$

Drop-out Voltage (cont'd)


Current Boost - Drop-Out Voltage

LDO Test - Experimental Results

 


Load Regulation
 
$$R_{o-reg} = \frac{\Delta V_{LDR}}{\Delta I_o} = \frac{R_{o-pass}}{1 + A_{ol}\beta}$$



- The load regulation performance is determined by **the open-loop gain** of the system
 - Unfortunately, the dc gain **is limited** by the frequency response of the regulator
- The **UGF**, in particular, is determined by
 - **The maximum allowable response time**
 - **The frequency range** where **the parasitic poles** of the system reside, such as the **internal poles** of the error amplifier

Pole/Zero Pair Generation

 


- Add a pole/zero pair
 - For a given unity gain frequency (UGF), the upper limit of the open-loop gain can be increased by manipulating the frequency response as depicted by trace B
 - The basic idea is for the gain to drop quickly as the frequency increases so that a larger dc gain is possible
 - Regulation is improved while keeping the UGF away from parasitic poles
- The fact that P_2 and Z_1 track each other can be used to optimize the design

AC simulation of LDO with an additional pole/zero pair



Macro1 - Open-loop Frequency Response

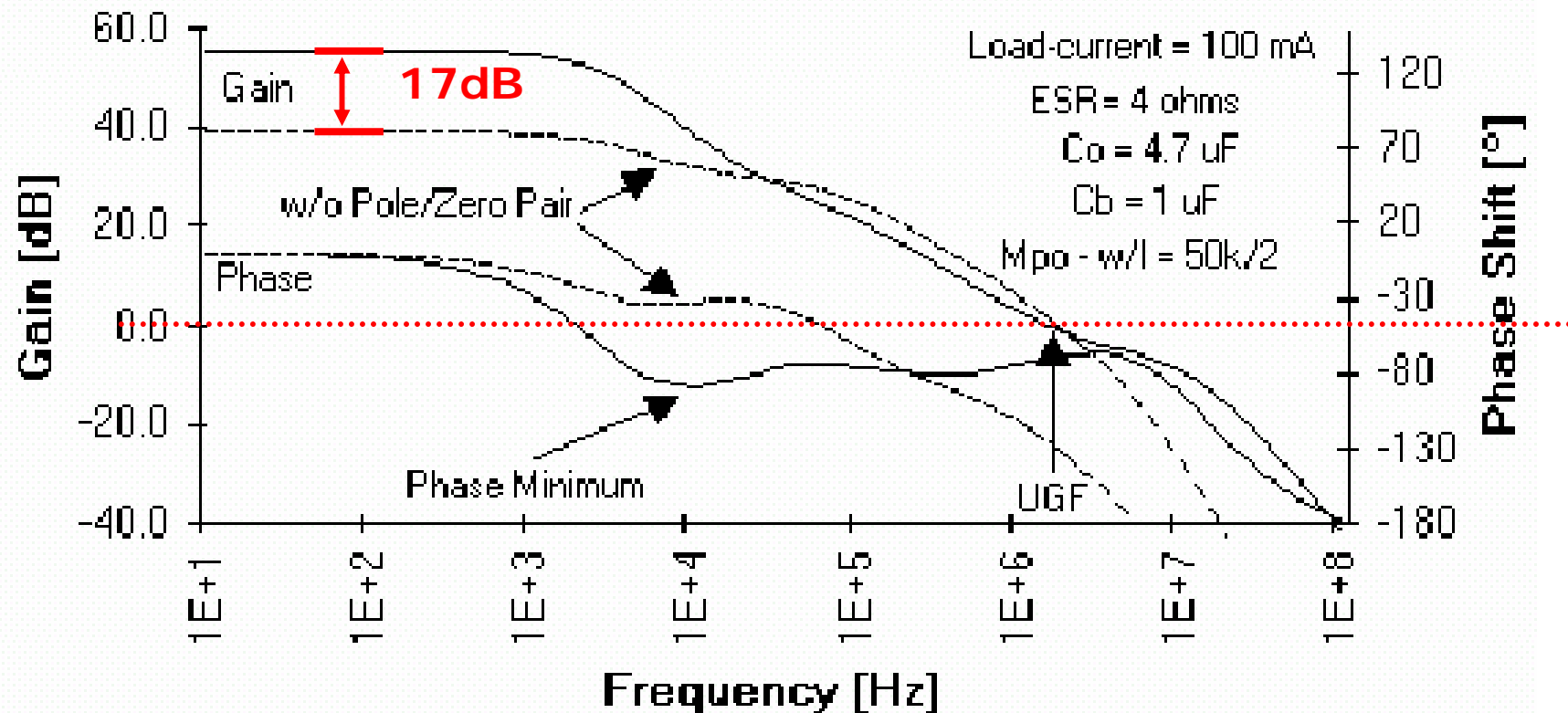Simulation Results - LDO with Additional Pole/Zero Pair



- Load regulation performance improved from approximately 41 to 12mV/100mA, corresponding to a 71% reduction

Parallel Amplifier Structure

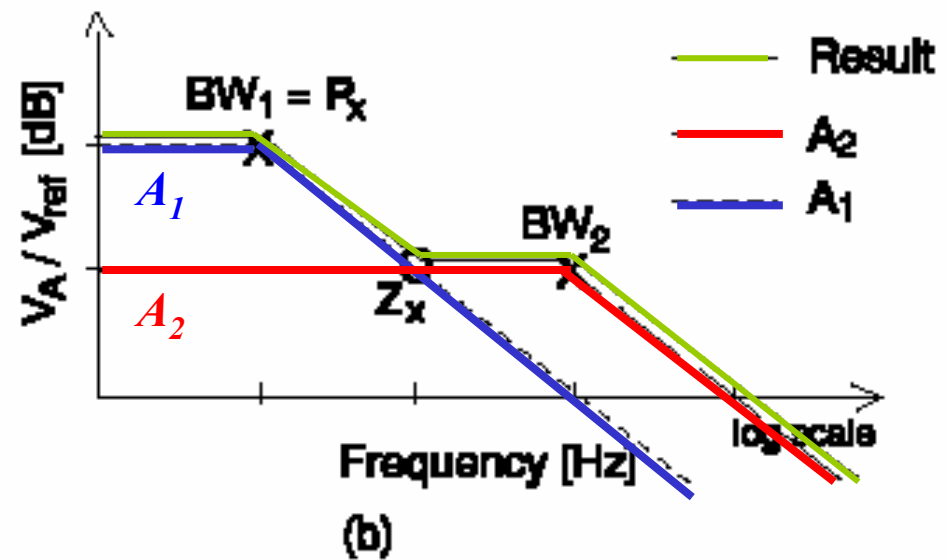 

Frequency Shaping Amplifier


- The main disadvantages of the Parallel Amplifier Structure
 - The circuit is **complexity**
 - The realization of the two amplifiers may prove to be costly in terms of **quiescent current flow**
- A pole/zero pair can also be generated through the use of **a feed-forward capacitor in a folded topology**
 - **At low frequencies**, the amplifier is **unaffected** by the feed-forward capacitor (C_{ff})
 - The gain is that of a typical **folded topology**, which is characteristically high
 - **At high frequencies**, the capacitors acts like an electrical **short**
 - Give rise to the gain of a **non-cascoded** architecture (**lower gain**)

Another realization of the Frequency Shaping Amplifier


- The circuit takes advantage of the **input and the output impedance of the mirror load**, composed of M_{p4} and M_{p5} , to **help shape** and define the frequency response of the amplifier

$$Z_X = \frac{1}{2\pi \left\langle R + \frac{1}{g_{m5}} \right\rangle C}$$
 
$$\text{and } P_X = \frac{1}{2\pi \left\langle R + \frac{1}{g_{m5}} + r_{ds4} \right\rangle C}$$




Circuit Design: Block Level Diagram

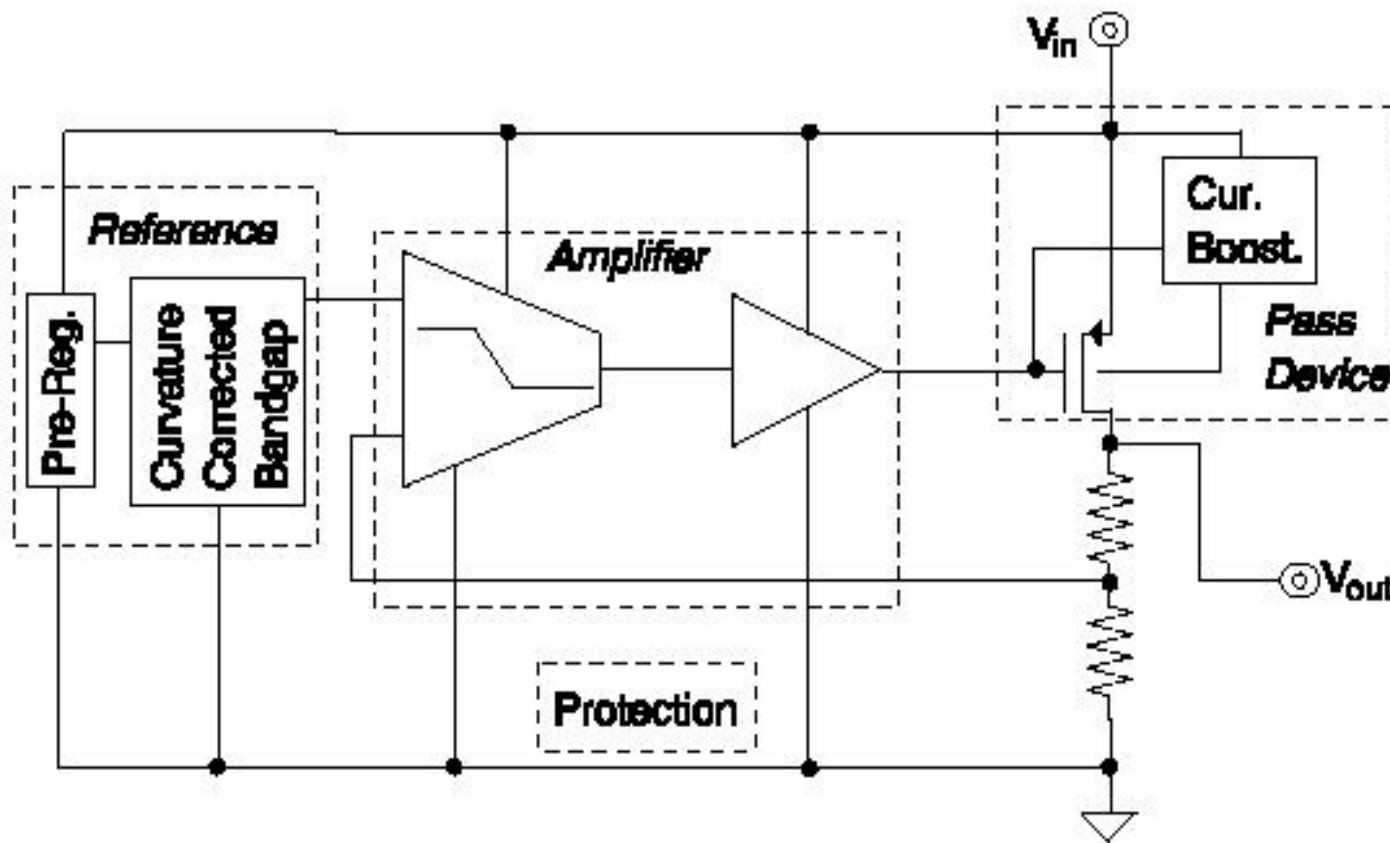


Pass Device


Basic configurations :

 


NPN Darlington

 


NPN

 

PNP

 


NMOS

 

PMOS

Pass Device (cont'd)

- Use **schottky diode**
 - $|V_{SB}|$ increase
 - $|V_{tp}|$ decrease
 - Can use **lower V_{in}** to drive M_{po}
- **Problem:**
 - During drop-out condition, M_{ps} and M_{po} are in different regions of operations. (**V_{sd} are different**)

 


Pass Device (cont'd)

Solution : make V_{sd} of M_{ps} and M_{po} to be equal


(b) $V_{in} > V_{sd-Mps} + V_{ec-Qp1} + V_{gs-Mirror}$

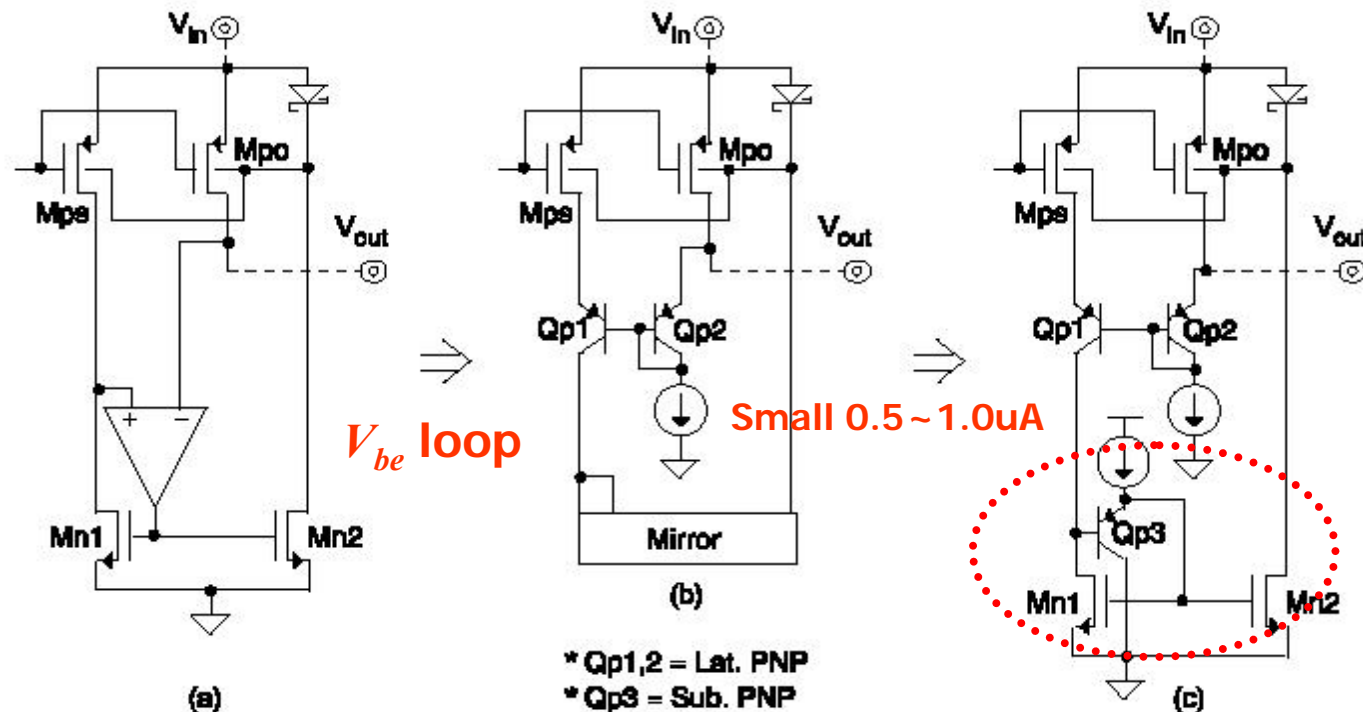(c) $V_{in} > V_{sd-Mps} + V_{ec-Qp1} + V_{gs-Mirror} - V_{eb}$



Amplifier (cont'd)

 - Buffer :
 - A low input capacitance for gain stage
 - A low output impedance for pass-element
 - Q_{n1} : a class A NPN emitter follower



Amplifier (cont'd)

□ Gain stage :


- Use NPN transistor to be the differential pair

- NPN: $V_{be} = 0.6 \sim 0.7$


- MOS: $V_{gs} = 0.9$

- (a): $V_{in} > V_{sg} + V_{ce} + V_{ds}$

- (b): $V_{in} > V_{sg} + V_{ds}$

 


$$V_{sg} - V_{be} \sim 0.2v$$

 


Reference

- M_{pp1} will turn into **Triode region**
- $T \downarrow$; $V_{be} = V_{dg} \uparrow \uparrow > |V_{th}| \uparrow$
- This causes the **temperature stability** of the reference to be **degraded**
 - $V_{be} : -2mV/K$
 - $V_{th} : \text{greater than } -2mV/K \text{ (about } -1.4mV/K)$

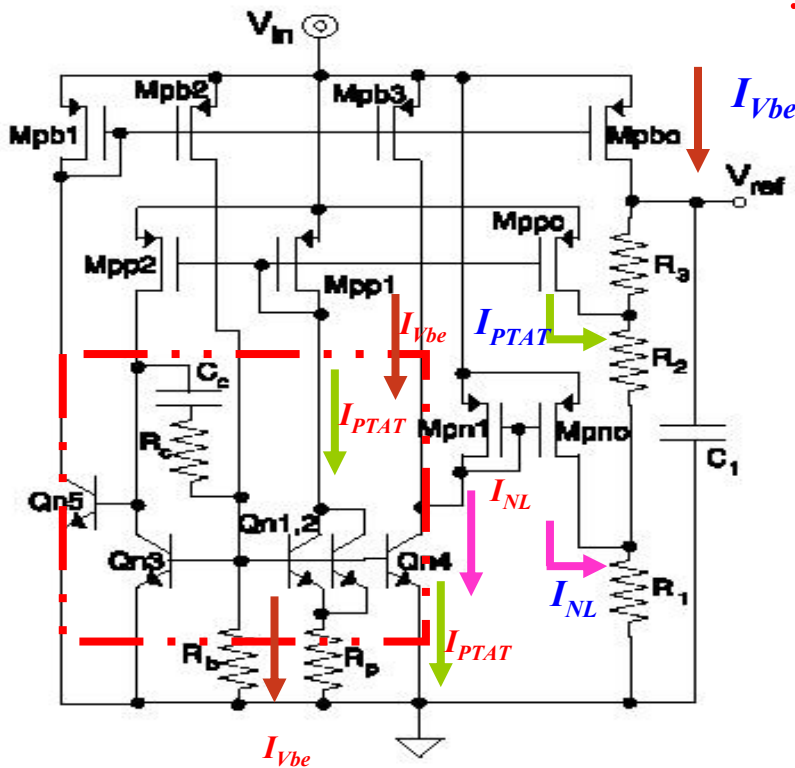


 
$$V_{in-min} = V_{sg-Mpp1} + V_{ce-Qn1} + V_{Rp}$$




$$V_{in-min} = V_{sg-Mpp1} + V_{ds-Mn1}$$

Reference (cont'd)

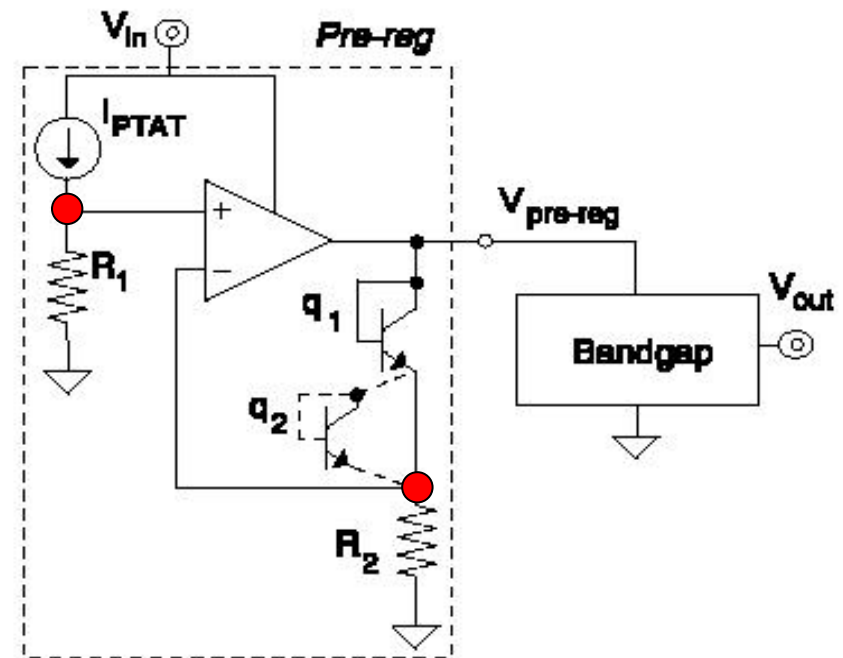 
- Line regulation enhancement
 - Provide a first order voltage-mode bandgap reference



The Whole Chip

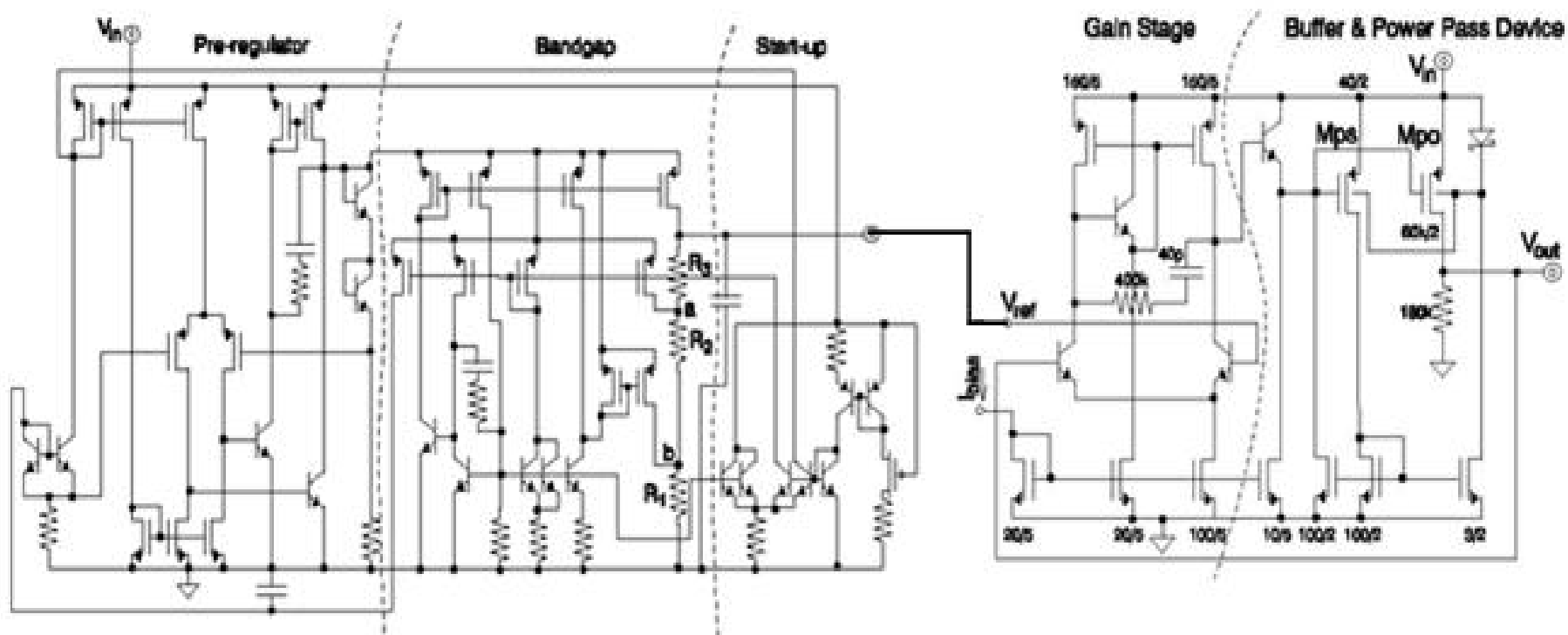

Typical LDO Voltage Regulator

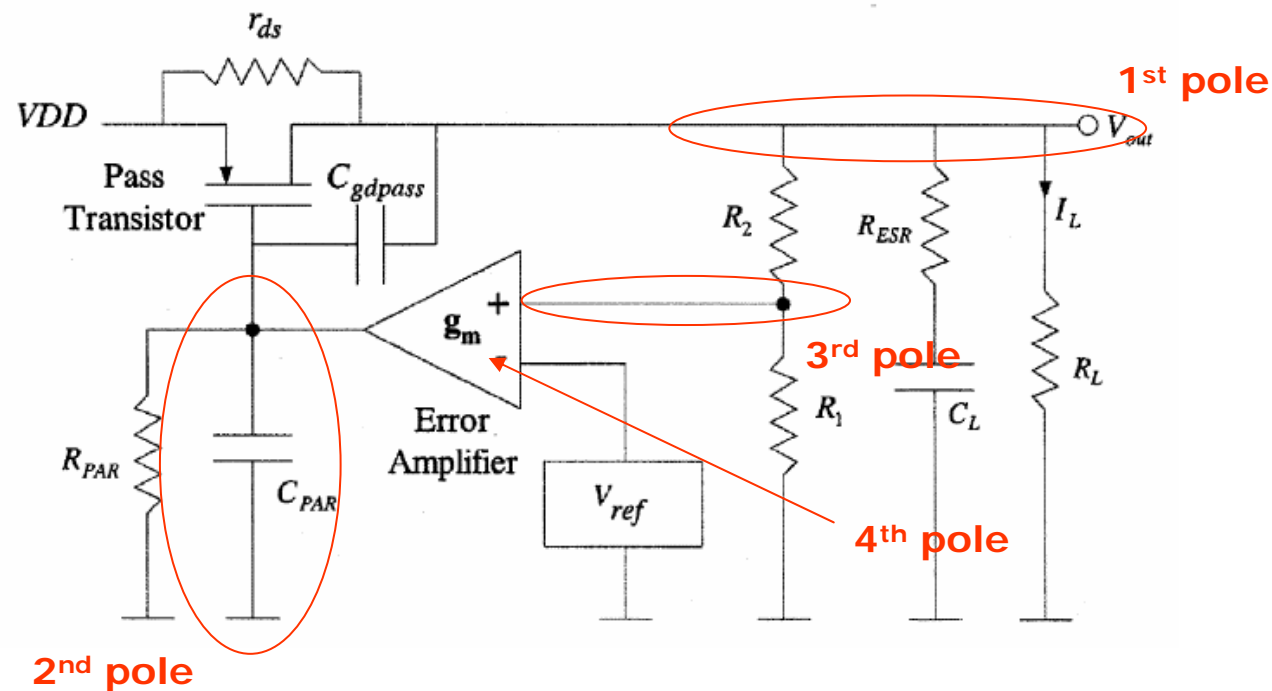

- ❑ The impedance seen from drain is inversely proportional to load current, so ***pole is heavily dependent on load condition***
- ❑ A solution is to **introduce a zero** that compensates to guarantee ***phase margin better than 45 degrees***
- ❑ In a conventional LDO, **ESR of output capacitor** generates this zero

Open-loop gain transfer function


$$H(s) \cong \frac{A_0 \left(1 + \frac{s}{\omega_{ESR}}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

$$A_0 = (g_m R_{par}) \cdot \left[g_{mpass} (r_{ds} \parallel (R_1 + R_2) \parallel R_L) \right] \cdot \frac{R_1}{R_1 + R_2}$$

$$\omega_{ESR} = \frac{1}{R_{ESR} C_L}$$

$$\omega_{p1} \approx \frac{1}{(r_{ds} \parallel (R_1 + R_2) \parallel R_L) C_L}$$
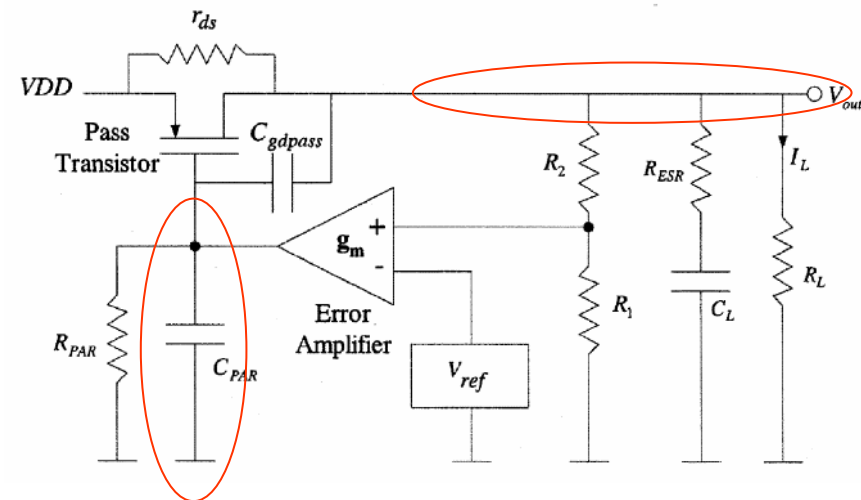
$$\omega_{p2} \approx \frac{1}{R_{par} [C_{par} + (1 - A_v) C_{gdpass}]} \approx \frac{1}{R_{par} [C_{par} + g_{mpass} (r_{ds} \parallel (R_1 + R_2) \parallel R_L) C_{gdpass}]}$$



- There is **no simple rule** to decide the exact location of the zero
- The zero **must be located below** the unity gain frequency
- **All high frequency poles** must be located **at least three times** the unity gain frequency

RHP Zero and Two Dominant Poles

- A more detailed analysis shows that a **right-hand side zero** is also present

$$V_{in} g_{mpass} = s V_{in} C_{gdpass} \Rightarrow s = \frac{g_{mpass}}{C_{gdpass}} (RHP) \quad \blacksquare \text{ Can easily be placed at high frequency}$$


- C_{gdpass} **links the two dominant poles**

assume $C_L \gg C_{gdpass}$ and $R_{LT} = r_{ds} \parallel (R_1 + R_2) \parallel R_L$

$$\omega_{p1,2} \approx \frac{1 \pm \sqrt{1 - 4 \frac{1}{R_{PAR} R_{LT} (C_{PAR} + C_{gdpass}) C_L} \left(\frac{1}{R_{PAR} (C_{PAR} + C_{gdpass})} + \frac{1}{R_{LT} C_L} + \frac{g_{mpass} C_{gdpass}}{(C_{PAR} + C_{gdpass}) C_L} \right)^2}}{2 \left(\frac{1}{R_{PAR} (C_{PAR} + C_{gdpass})} + \frac{1}{R_{LT} C_L} + \frac{g_{mpass} C_{gdpass}}{(C_{PAR} + C_{gdpass}) C_L} \right)}$$


ESR Compensation

- ❑ The ESR is **not properly specified** and **varies with temperature**
 - The **high-frequency bypass capacitors** placed in parallel with the output capacitor form a pole **further decrease the phase margin**
- ❑ Ceramic capacitors are **cheaper** than tantalum capacitors, but ESR of ceramic capacitors typically **less than 0.05 ohm**
 - ESR **increases the overshoot drastically** if large resistors are used

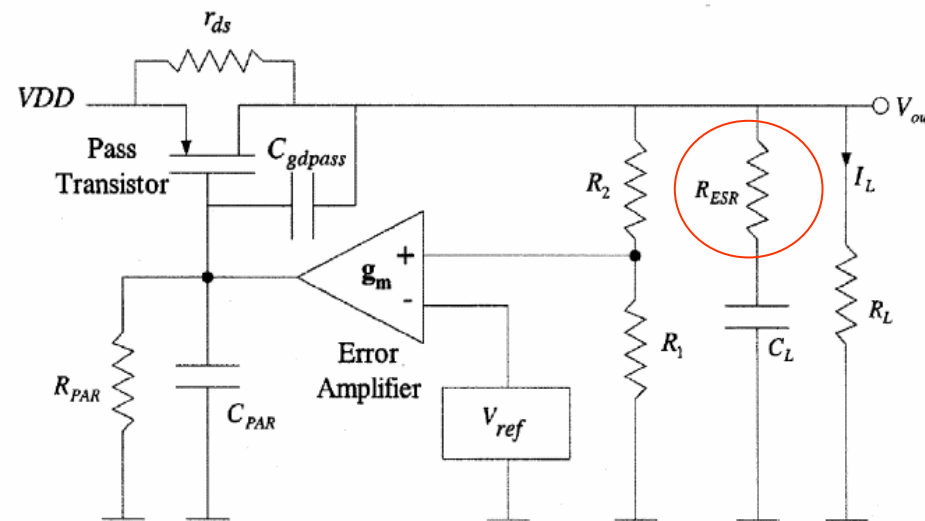

Use Charge Pump Booster

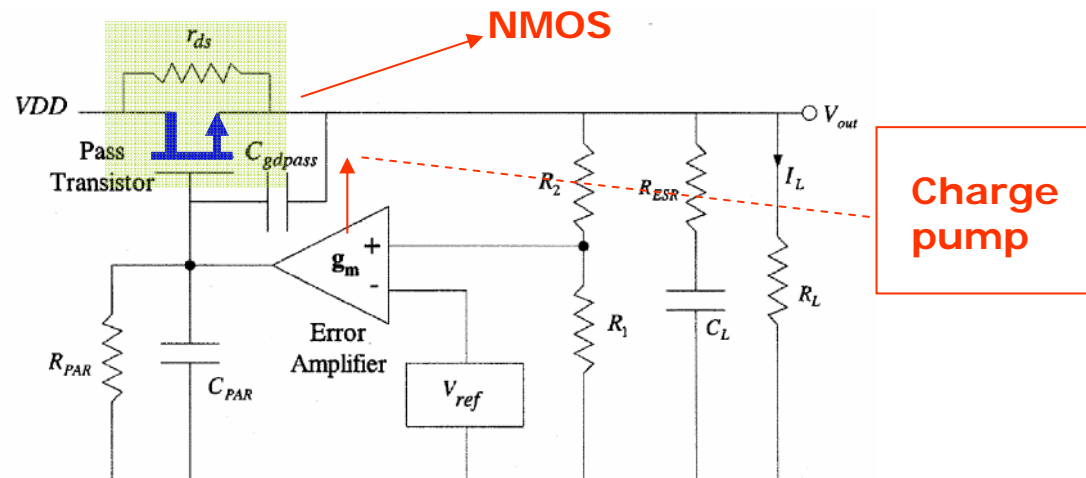- ❑ Generates a voltage higher than the supply than the supply voltage and the EA utilizes the voltage
 - Provides low output impedance
- ❑ Additional circuitry
 - Power consumption & noise performance
- ❑ Due to higher voltage generated, might not be well suited for advanced tech (because of HV process)




Pole-Splitting

- ❑ Miller capacitor **must be huge** to push **the LDO output pole beyond the unity gain frequency**
- ❑ Miller capacitor with C_{gs} of pass transistor forms a direct path **for power supply spurs to output**
 - The circuit has to be modified to **have an extra buffer stage** and this modification introduces additional parasitic poles
- ❑ **Disadvantages** of Miller compensation:
 - Reduces bandwidth, slew rate
 - Need more power, area
- ❑ The topology that creates the zero **by using feedforward techniques** but still Miller techniques are employed

Capacitive Feedback

- Basic idea is to introduce a left-hand plane (LHP) zero in the feedback loop that would replace the zero generated by ESR of the output capacitor
 - Advantages:
 - Precisely controlling the zero
 - Minimize the overshoots
- Add a pole-zero pair:
 - Zero at lower frequency than the pole
 - A drastic improvement in phase margin can be obtained by adding only a zero
 - Previous design added an internal zero by using a series resistor and capacitor combination connected to the output of EA

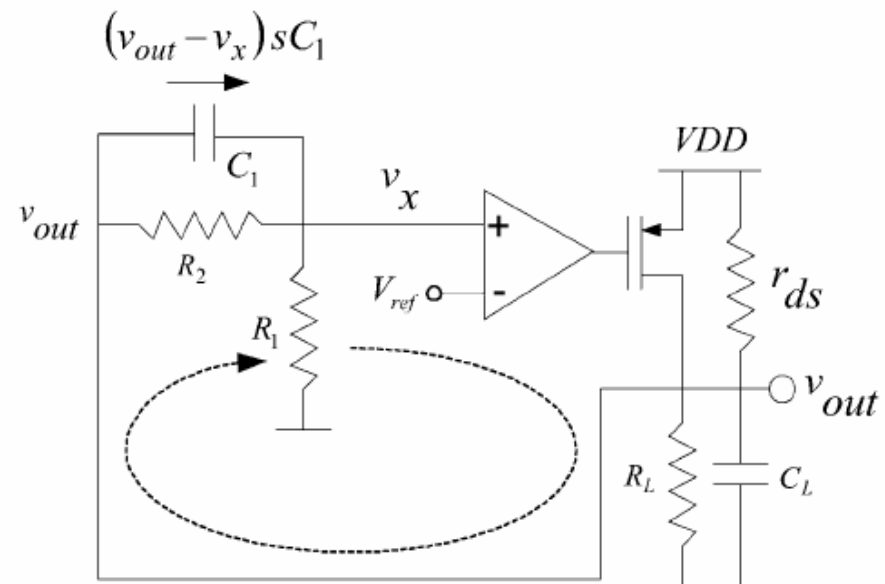

Capacitive feedback (cont'd)

Open-loop gain transfer function

$$H(s) \cong \frac{A_0 \left(1 + \frac{s}{\omega_{z1}}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \left(1 + \frac{s}{\omega_{p3}}\right)}$$

- ω_{p3} is not far away from the zero
- The topology has to be modified so as to eliminate ω_{p3} without affecting the zero

$$A_0 = (g_m R_{par}) \cdot \left[g_{mpass} (r_{ds} // (R_1 + R_2) // R_L) \right] \cdot \frac{R_1}{R_1 + R_2}$$

$$\omega_{z1} = \frac{1}{R_2 C_1} \left[-v_x s C_1 - \frac{v_x}{R_2} = 0 \Rightarrow s = -\frac{1}{R_2 C_1} \right]$$



$$\omega_{p1} \approx \frac{1}{(r_{ds} // (R_1 + R_2) // R_L) C_L}$$

$$\omega_{p2} \approx \frac{1}{R_{par} [C_{par} + (1 - A_v) C_{gdpass}]} \approx \frac{1}{R_{par} [C_{par} + g_{mpass} (r_{ds} // (R_1 + R_2) // R_L) C_{gdpass}]}$$


$$\omega_{p3} = \frac{1}{(R_1 // R_2) C_1} = \frac{1 + \frac{R_2}{R_1}}{R_2 C_1} \longrightarrow 1.33$$

VCCS Method

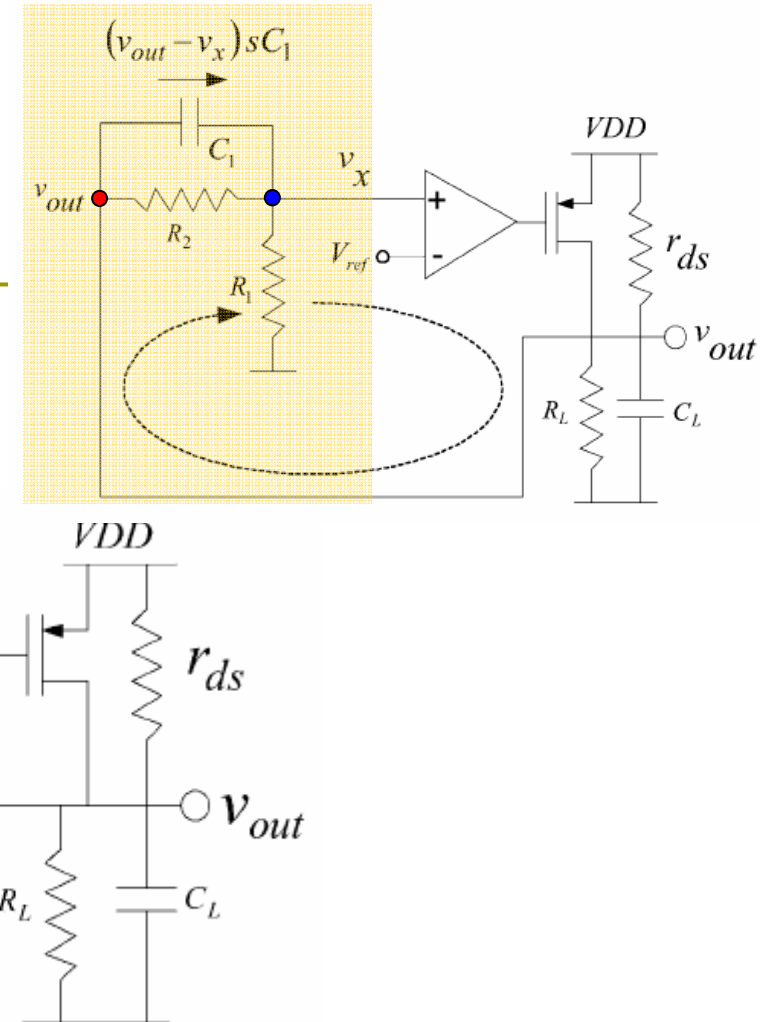 A drastic improvement in phase margin can be obtained **by adding only a zero**



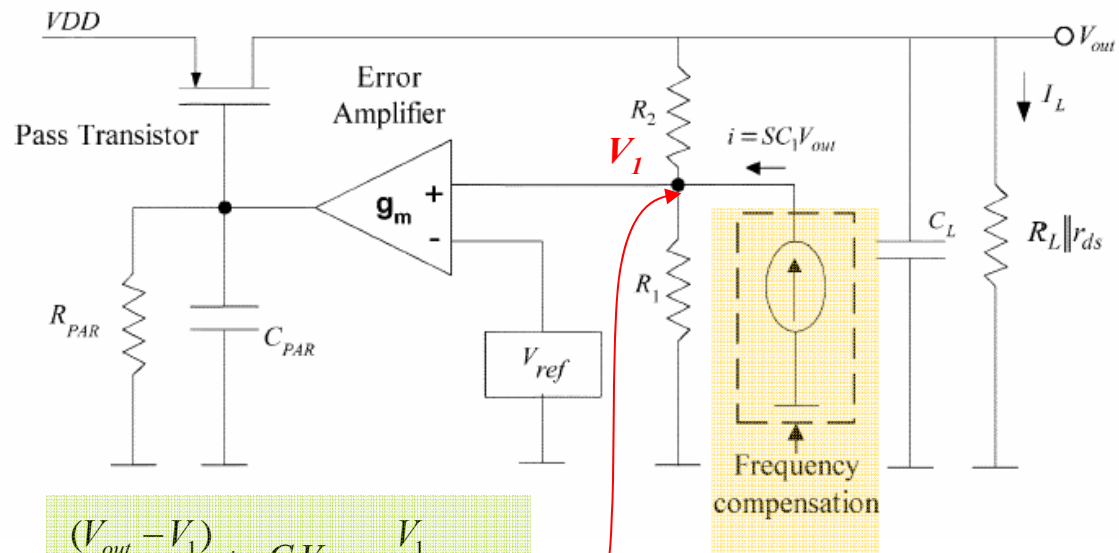- C_1 & $VCCS$ connected to v_{out} **do not significantly** alter the voltage at that node since C_L is of **several μF** , whereas C_1 is on the order of few pF
- The capacitor connected to v_x **is responsible for the additional pole ω_{p3}**
- The $VCCS$ is a **differentiator** that increases the loop gain



$$\omega_{z1} = \frac{1}{R_2 C_1}$$

$$\omega_{p1} \approx \frac{1}{\left(r_{ds} \parallel (R_1 + R_2) \parallel R_L \right) \left(C_L - \frac{C_1}{1 + \frac{R_2}{R_1}} \right)}$$

$$\frac{(V_{out} - V_1)}{R_2} + sC_1 V_{out} = \frac{V_1}{R_1}$$

$$V_1 = (R_1 \parallel R_2) \left(sC_1 + \frac{1}{R_2} \right) V_{out}$$

$$\text{Thus: } \frac{V_{out} - V_1}{R_2} = \frac{V_{out} \left[1 - (R_1 \parallel R_2) \left(sC_1 + \frac{1}{R_2} \right) \right]}{R_2} = V_{out} \left[\frac{1}{R_1 + R_2} - \frac{R_1}{R_1 + R_2} sC_1 \right]$$

$$\omega_{p2} \approx \frac{1}{R_{par} \left[C_{par} + (1 - A_v) C_{gdpass} \right]} \approx \frac{1}{R_{par} \left[C_{par} + g_{mpass} \left(r_{ds} \parallel (R_1 + R_2) \parallel R_L \right) C_{gdpass} \right]}$$

- Pole is **almost not altered** by C_1
- This circuit **works only with low ESR capacitors** as co-existence of V_{CCS} generated zero and ESR generated zero at low frequencies **might make loop gain undesirably high**

Parasitic Pole of VCCS Schematic



$$Z_{in} = \frac{V_{out}}{i_{out}} = \frac{1}{g_{m1} + sC_1} = \frac{1/C_1}{g_{m1}/C_1 + s}$$

pole is at $\frac{g_{m1}}{C_1}$

around 400kHz for $I_B = 0.5\mu A$ & $C_1 = 5pF$

- Push parasitic pole beyond 1MHz for $C_1 = 25pF$ (required for the proper location of the zero)


- We need to improve effective g_{m1}

  

$$G_m = A_{VOTA} \cdot g_{mx}$$


Increase the effective capacitance from 5 to 25pF

Reduced Z_{in}

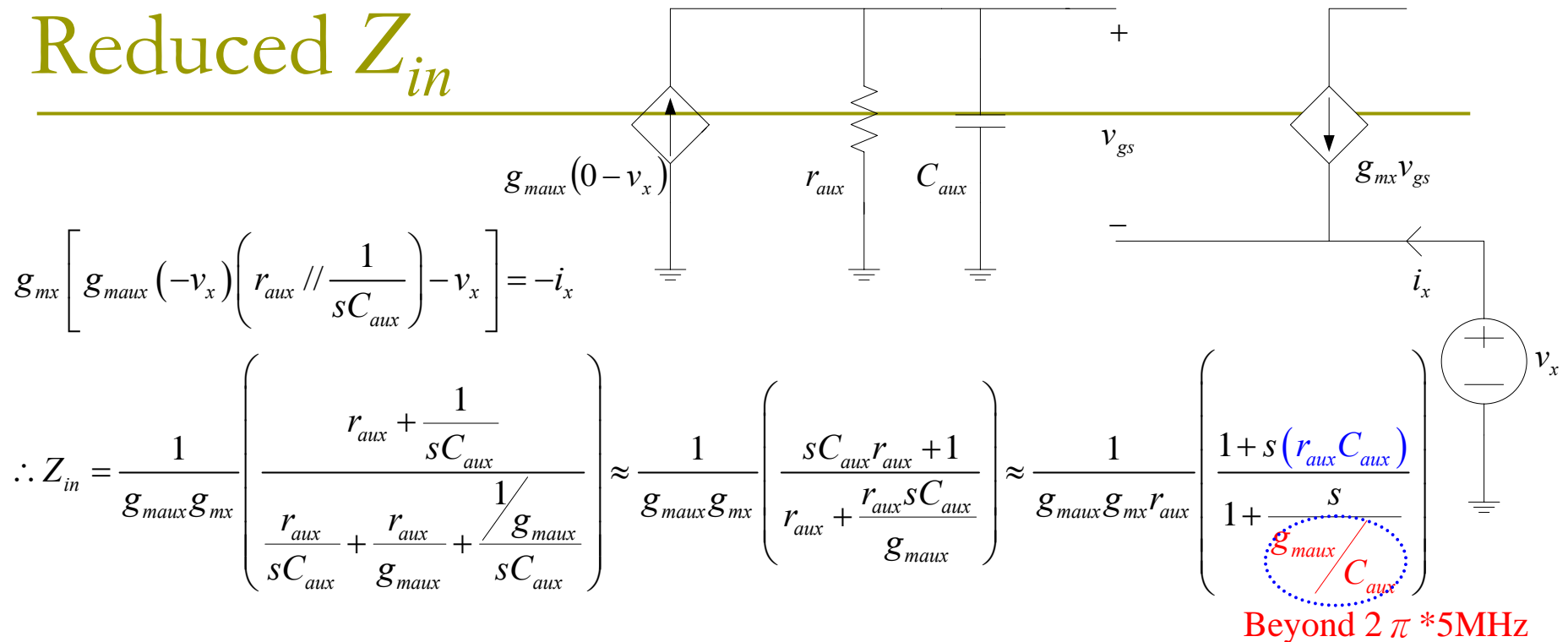


- The input impedance is **very small at low frequencies**, **collecting all current generated by C_1**
 - It is mandatory to **reduce $r_{aux} C_{aux}$** to extend the frequency capabilities
- At high frequencies, the Z_{in} **increases to $1/g_{mx}$** ; if $|Z_{in}| \ll 1/\omega C_1$, the circuit can properly drive C_1 (since the pole is at $sC_1 Z_{in} + 1 = 0$)

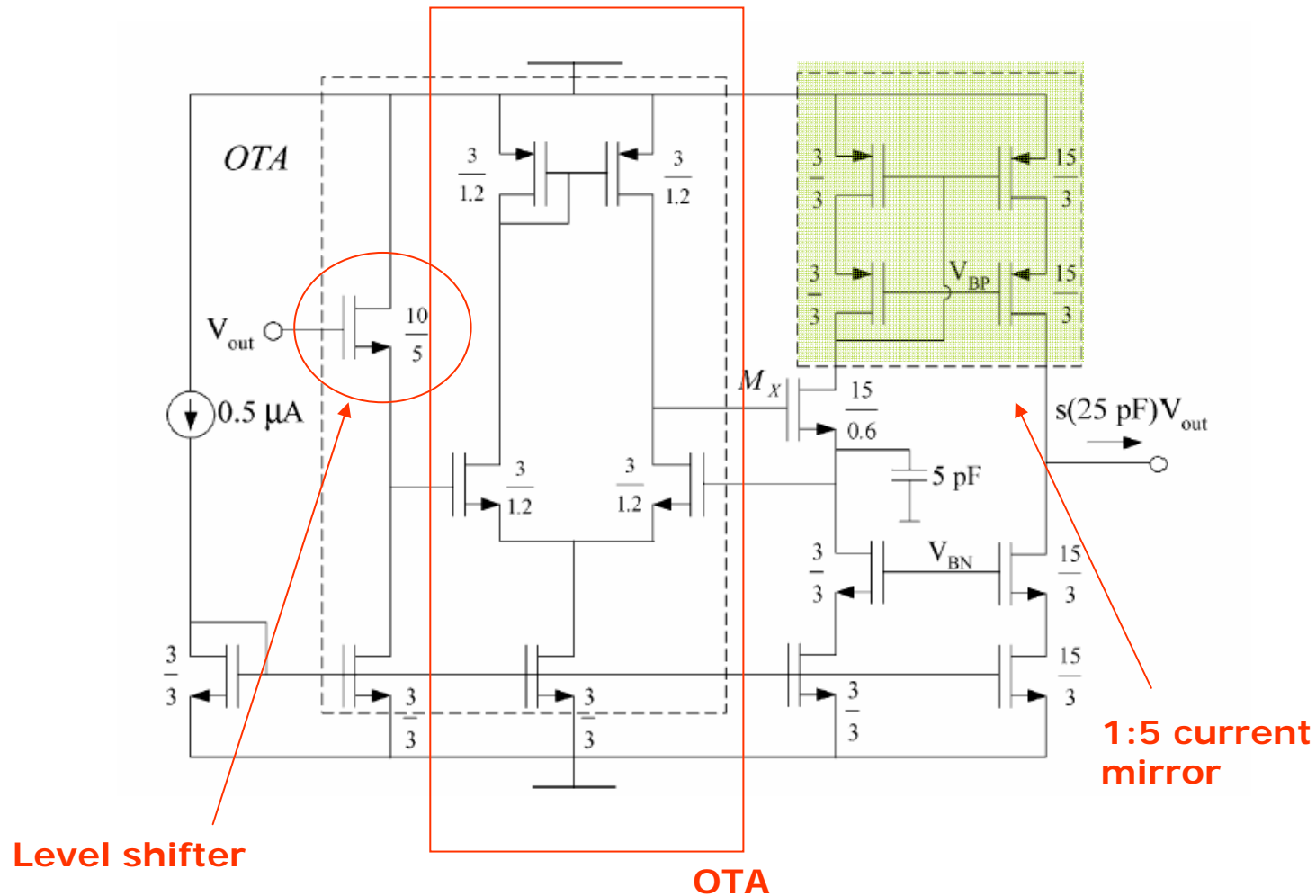Transistor level implementation of VCCS with GM enhancement




Error Amplifier

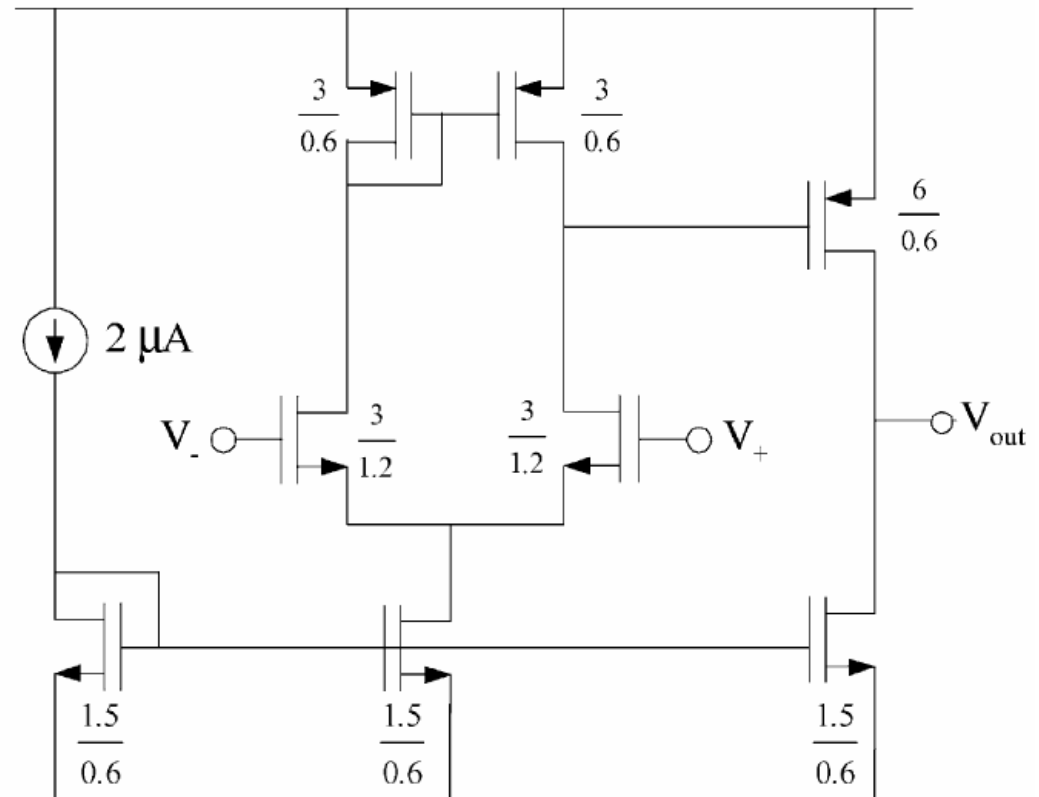


- High dc gain ($>60\text{dB}$) for all loads
- Low output impedance to keep the pole at the input of the pass transistor at high frequencies
- Positive rail output to turn off pass transistor
- Internal poles at significantly higher frequencies compared to cross over loop frequency

Open-loop Gain

 - $R_1=120k\ \text{ohm}$, $R_2=160k\ \text{ohm}$
- $V_{dd}=3.3V$, $V_{ref}=1.2V$
- $C_L=2.2\mu F$
- $ESR\ \text{of}\ C_L < 100m\ \text{ohm}$
- Dc output is $2.8V$
- Current consumed by LDO is $25\mu A$
- Current consumed by VCCS is $5\mu A$
- Unity gain frequency is in $250 \sim 650kHz$
- Phase margin $> 60\ \text{deg}$




Load Regulation

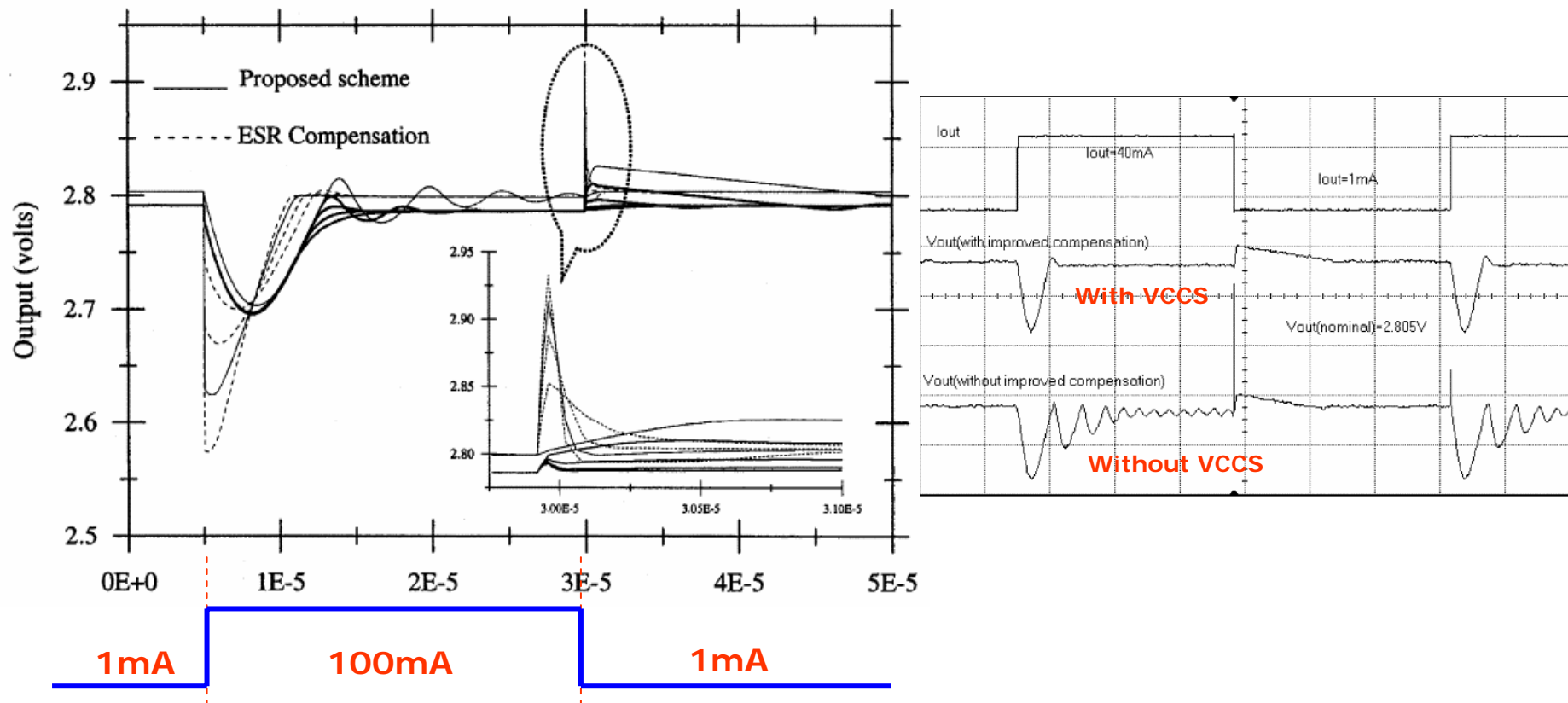


- The compensating circuit is a differentiator, it helps increasing the loop feedback for fast output variations
- ESR increase overshoots

Line Regulation

 

- At low frequencies, line regulation (power supply rejection) of the regulator is determined by the loop dc gain since VCCS does not change the loop gain
- High-frequency line regulation is not degraded since VCCS does not add any significant parasitic capacitance from supply voltage to the output

Start-up Time


 


Load current=5mA

- The proposed circuit **has similar start-up time** compared to the scheme with **ESR generated zero**
 - The speed limitation comes from the fact that the VCCS **has an ideal behavior up to a few megahertz**
 - The start-up behavior could be slight different for both cases depending upon **high-frequency behavior of the VCCS**


Noise Response

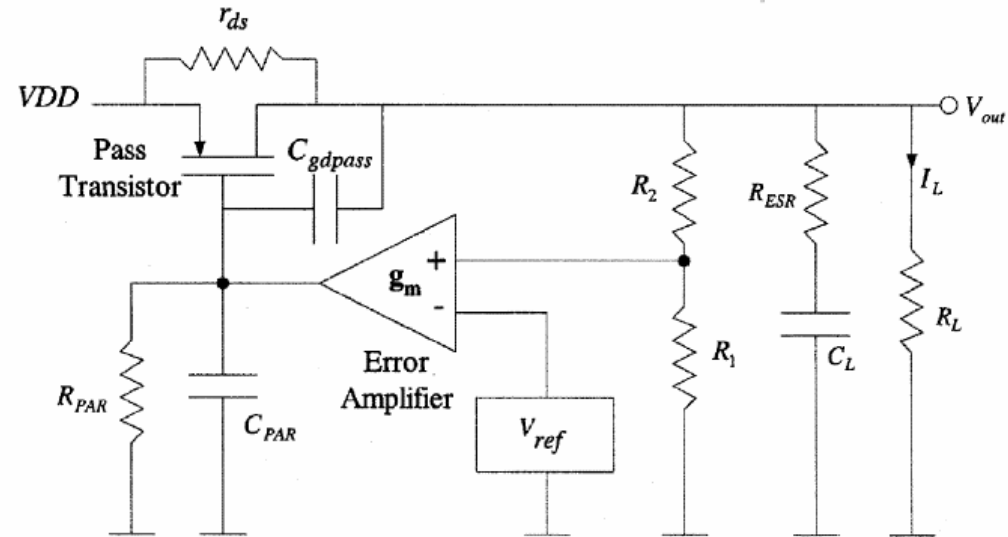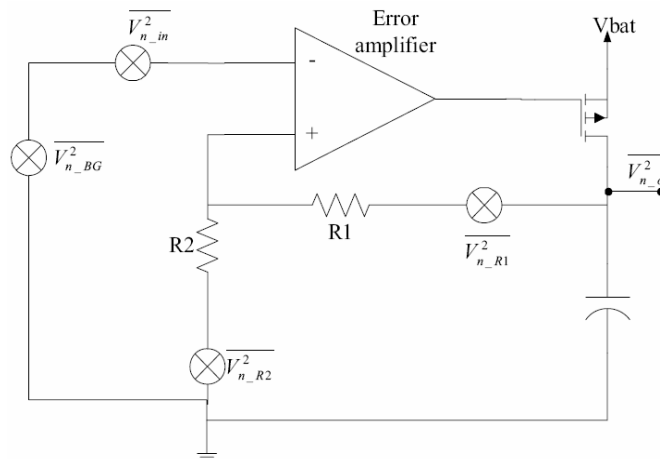- Four noise components :
 - V_{ref} generator
 - EA
 - Pass transistor
 - Feedback resistor




$$\left| \frac{v_{out} / v_{ref, proposed}}{v_{out} / v_{ref, ESR}} \right| = \left| \frac{1}{1 + \frac{s}{\omega_{ESR}}} \right|$$

 
- The zero is generated by additional circuitry (lumped to the VCCS) **that is not in the direct path of the noise transfer function**
- The high-frequency noise due to the V_{ref} generator, EA, pass transistor is therefore **attenuated**



1.2mV

 


936uV

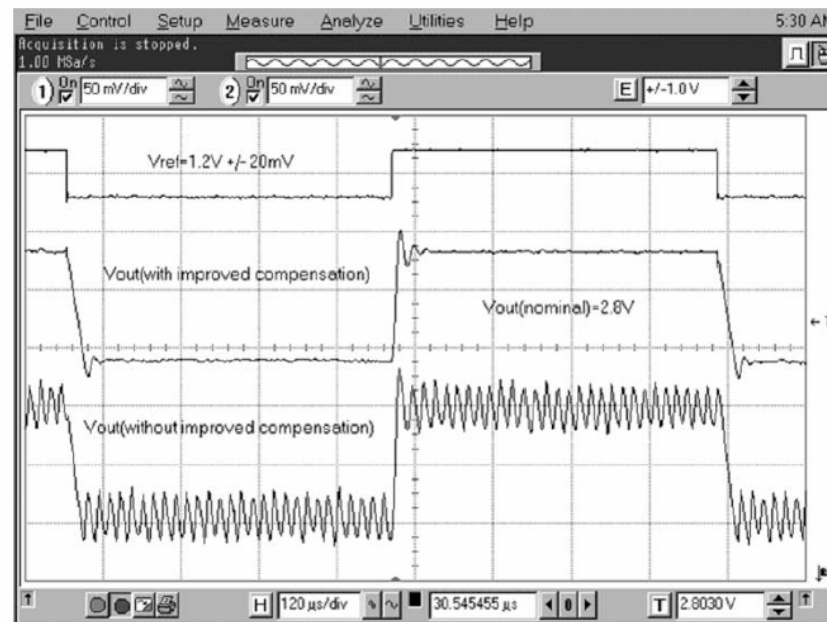

With VCCS

Without VCCS

Output Voltage vs. Load Current

 


- Loop gain increases further for very small current (pass transistor go into subthreshold region and the output resistance of both pass transistor and load increase)
- Another voltage drop in the output voltage occurs when the pass transistor goes into triode region thereby reducing the open-loop gain

Structure of Generic CMOS LDO

- There are two poles and one zero:

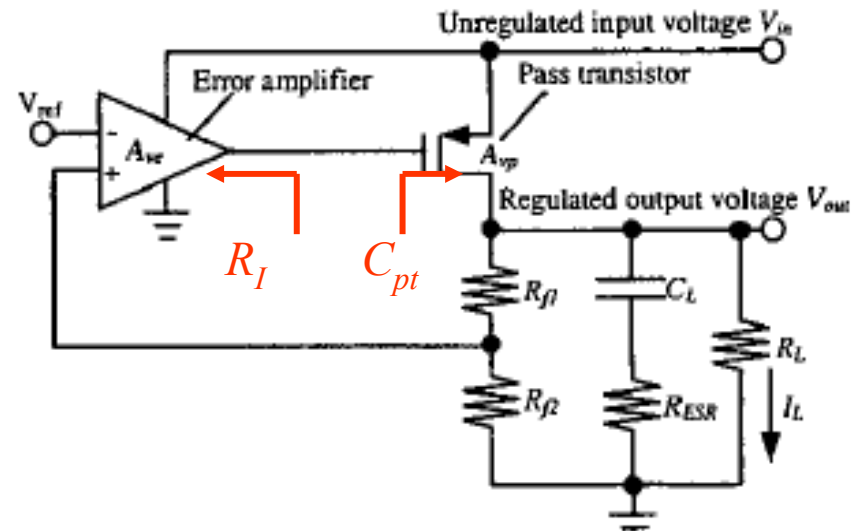
- $p_1 = 1/C_L(R_L + R_{esr})$
- $p_2 = 1/C_{pt}R_I$
- $Z_{esr} = 1/C_L R_{esr}$



- The pass transistor is CS configuration with negative voltage gain, the feedback signal is connected to positive input of the error amplifier in order to achieve negative feedback loop
- Voltage reference is commonly using a bandgap reference that can work below 5V (The others are zener and buried-zener voltage)

Stability of LDO using Dominant-Pole Compensation

 
- The **smaller ESR** has the **better load transient performance** that is **less overshoots and undershoots**
 - The ESR zero would not be involved since it locates at a very high frequency
- The dominant pole p_1 is located at a very low frequency, so the required value of C_L is huge



Stability of LDO using Dominant-Pole Compensation (cont'd)


- ❑ The dominant pole p_1 is shifted to higher frequency(p_1') for a higher load current and the LDO may be unstable at a certain load
 - P_2 may locate before the unity-gain frequency
 - The generic LDO should be compensated at the maximum load current (worst case)
 - The unity-gain frequency of loop gain is constrained by p_2 ,
 - ❑ B.W. is small, loop response is slow.. ($p_2=1/C_{pt}R_l$)
- ❑ The LDO using the dominant-pole compensation usually has a narrow Bandwidth and requires a huge capacitor

Stability of LDO using Buffer

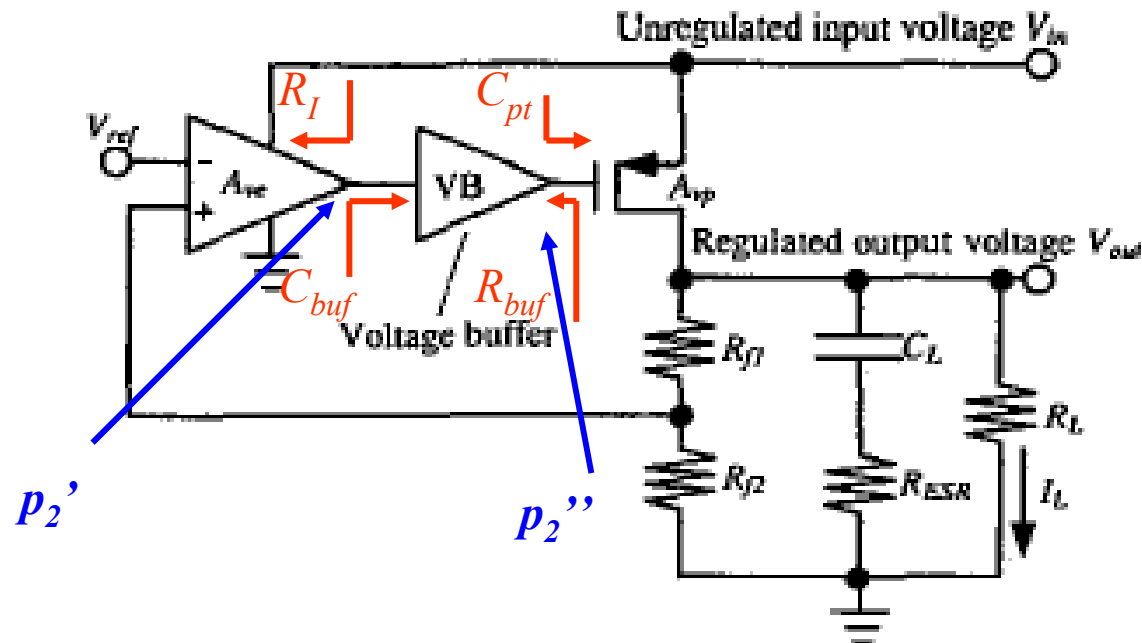

- In order to increase the UGF, a buffer stage can be interposed between the output of the error amplifier and input of the power pass transistor
 - The low frequency p_2 is split into two higher frequency poles p_2' and p_2''
 - $p_2' = 1/C_{pt}R_{buf}$, $p_2'' = 1/C_{buf}R_I$

Stability of LDO using Buffer (cont'd)

 


- p_2' and p_2'' are much higher than p_2 , because the value of C_{pt} is usually quite large (due to power MOS), therefore p_2' is lower than p_2''
- Since the two split poles are at much higher frequencies, a small C_L can be used where the new dominant pole p_1'' is at a higher frequency, the UGF of LDO increases

Problems of LDO with Buffer in Low-Voltage Design

- A simple way to implement the buffer stage is use a PMOS or NMOS in source-follower
 - There is one V_{GS} drop across the buffer, for low-voltage design ($V_{in} \sim 1.2V$), the power pass transistor can't be either
 - Fully turned ON (using PMOS buffer) or
 - Fully turned OFF (using NMOS buffer)
 - If the buffer implemented by PMOS transistor, when I_L increases the output transistor of the error amplifier are forced **to operate in triode region**
 - So R_f decreases and loop gain decreases
 - Due to reduction of the loop gain, **the performance of the load regulation, line regulation and load transient would be greatly degraded**

Advantage and Stability of Nested Miller Compensation for Low-Voltage LDOs

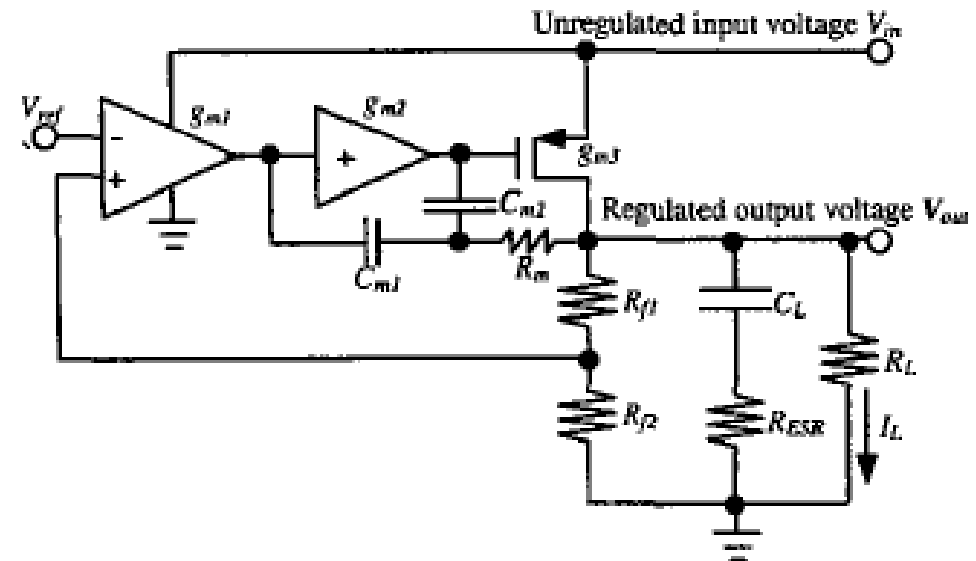- An error amplifier with two gain stages is used to provide a sufficient voltage gain (g_{m1} , g_{m2})



- Nested Miller compensation technique with nulling resistor (R_m) is used to achieve stability (*Cancel Zero*)
- Compensation capacitors C_{m1} and C_{m2} are $4pF$ and $1pF$, respectively
- No large filtering capacitor C_L is required, the whole LDO including the C_L can be integrated into a single chip

Compare three Compensation Type

- Parameters of the LDO with different compensation scheme

	Generic LDO	LDO with a buffer	Three-stage topology
V_{dd}			
C_L	$5\mu F$	$0.1\mu F$	$100pF$
R_{ESR}	$20m\Omega$	$20m\Omega$	
C_{m1}, C_{m2}, R_m			$4pF, 1pF, 10\Omega$

- UFG, PM and low-frequency loop gain of the LDO in different compensation schemes

		$I_L=5mA$	$I_L=10mA$	$I_L=15mA$	$I_L=20mA$
Generic LDO	UGF	118kHz	162kHz	186kHz	200kHz
	PM	61°	53.4°	50.4°	49°
	A_o	62.4dB	59.6dB	56.4dB	52.9dB
LDO with buffer	UGF	1.53MHz	789kHz	418kHz	237kHz
	PM	60.9°	74.9°	83.3°	89.1°
	A_o	50.6dB	38.6dB	29.9dB	23.2dB
Three stage topology	UGF	4.47MHz	4.41MHz	4.37MHz	4.34MHz
	PM	42.3°	43.3°	43.5°	43.5°
	A_o	96dB	94.9dB	93.8dB	92.6dB

Nested Miller Compensation (NMC)

- The stability condition as per the separate pole approach is given by

$$GBW \leq \left(\frac{1}{2}\right) p_2 \leq \left(\frac{1}{4}\right) p_3$$

$$\Rightarrow (g_{m1}/C_{m1}) \leq \left(\frac{1}{2}\right) (g_{m2}/C_{m2}) \leq \left(\frac{1}{4}\right) (g_{mL}/C_L)$$

$$\Rightarrow C_{m1} = 4 \left(\frac{g_{m1}}{g_{mL}} \right) C_L \quad \text{and} \quad C_{m2} = 2 \left(\frac{g_{m2}}{g_{mL}} \right) C_L$$

This yields **large compensation capacitors** for **large load capacitors**

- Large load capacitors **limit the GBW to a great extent** as :

$$GBW = (g_{m1}/C_{m1}) = \left(\frac{1}{4}\right) \left(\overset{\uparrow}{g_{mL}} / C_L \right)$$

- **Smaller compensation capacitors are obtained for larger values of g_{mL}**


- Not suitable **for low-power design**, especially when driving large capacitive loads

SMC and SMFFC

- Two new amplifier topologies
 - SMC (**single** miller capacitor amplifier)
 - SMFFC (**single** miller capacitor **feedforward** frequency compensation amplifier)
- Advantages:
 - Only a small compensation capacitor (C_m)
 - **Small area**
 - Gain-bandwidth product is improved
 - Large signal and small signal performance is improved
 - Because of the reduction of the size of the compensation capacitor C_m
 - **No pole-zero doublets** in the passband for SMC
 - The **high-frequency pole-zero doublet** for SMFFC

Single Miller Capacitor Amplifier (SMC)

- Single Miller Capacitor Amplifier (SMC)
 - An additional transconductance stage, g_{mf} , from the output of the first stage to the final output
 - This **forms a push-pull stage** at the output that helps in *improving the transient response of the amplifier*
 - A single Miller compensation capacitor (C_m) is used to split p_1 and p_3
 - *A judicious distribution* of the total gain among the three stages can stabilize the amplifier
 - p_2 is dictated by the gain of the second stage

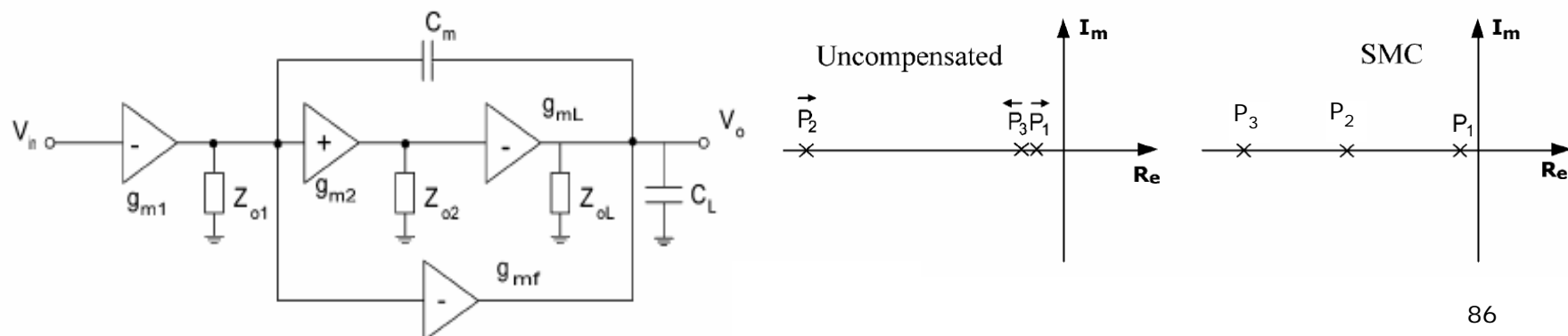

Small-Signal Analysis of SMC

$$z_1 = \frac{G_{meff}}{C_m} \text{ (RHP)}$$

$$z_2 = -\left(\frac{g_{p2}}{C_{p2}} + \frac{G_{meff}}{C_m}\right) \text{ (LHP)}$$

$$|z_2| > z_1 \gg p_{1,2,3}$$

Two high-frequency zeros

□ SMC

$$A_{v(SMC)}(s) = \frac{A_{dc} \left(1 + s \frac{C_{p2}g_{mf} - C_m g_{o2}}{g_{m2}g_{mL}} - s^2 \frac{C_m C_{p2}}{g_{m2}g_{mL}} \right)}{\left(1 + \frac{s}{P_{-3dB}} \right) \left(1 + s \frac{C_L g_{o2}}{g_{m2}g_{mL}} + s^2 \frac{C_{p2}C_L}{g_{m2}g_{mL}} \right)} \cong \frac{\left(1 + s \frac{C_{p2}g_{mf} - C_m g_{o2}}{g_{m2}g_{mL}} - s^2 \frac{C_m C_{p2}}{g_{m2}g_{mL}} \right)}{\left(\frac{s}{GBW} \right) \left(1 + s \frac{C_L g_{o2}}{g_{m2}g_{mL}} + s^2 \frac{C_{p2}C_L}{g_{m2}g_{mL}} \right)}$$

$$\text{where } A_{dc} = \frac{g_{m1}g_{m2}g_{mL}}{g_{o1}g_{o2}g_L}, \quad P_{-3dB} = \frac{g_{o1}g_{o2}g_L}{g_{m2}g_{mL}C_m}, \quad GBW = A_{dc} \cdot P_{-3dB} = \frac{g_{m1}}{C_m}$$

Three poles

$$\text{Closed-loop with unity-gain feedback } A_{cl(SMC)} \cong \frac{1}{1 + \left(\frac{sC_m}{g_{m1}} \right) \left(1 + s \frac{C_L g_{o2}}{g_{m2}g_{mL}} + s^2 \frac{C_{p2}C_L}{g_{m2}g_{mL}} \right)} = \frac{1}{a_0 s^3 + a_1 s^2 + a_2 s + a_3}$$

$$p_2 = \frac{g_{m2}g_{mL}}{C_L g_{o2}} = \frac{(A_{v2}g_{mL})}{C_L} = \frac{(G_{meff})}{C_L}, \quad p_3 = \frac{g_{o2}}{C_{p2}} - \frac{G_{meff}}{C_L}$$

1/p₂

1/p₂p₃

$$\blacksquare \text{ Stability: by Routh-Hurwitz Criterion } a_1 a_2 - a_0 a_3 > 0 \Rightarrow \frac{g_{o2}}{C_{p2}} > \frac{g_{m1}}{C_m} = GBW$$

Small-Signal Analysis of SMC (cont'd)

- The complex poles and hence **high frequency peaking** are avoided if

$$\left(\frac{g_{o2}}{C_{p2}}\right)^2 \gg \frac{4g_{m2}g_{mL}}{C_{p2}C_L} \Rightarrow A_{v2} = \frac{g_{m2}}{g_{o2}} < \frac{1}{2} \sqrt{\frac{g_{m2}C_L}{g_{mL}C_{p2}}}$$

$$\text{■ } GBW < \frac{1}{2} p_2 < \frac{1}{4} p_3 \Rightarrow \frac{g_{m1}}{C_m} \leq \frac{1}{2} \frac{G_{meff}}{C_L} \leq \frac{1}{4} \left(\frac{g_{o2}}{C_{p2}} - \frac{G_{meff}}{C_L} \right) \Rightarrow C_m = \frac{1}{2A_{v2}} \left(4 \frac{g_{m1}}{g_{mL}} C_L \right)$$



- Reduce the size of C_m by a factor of $1/(2A_{v2})$ (**Slewing better than NMC**)
 - The requirement of $g_{mL} \gg g_{m1}$ **no longer needs** to be satisfied
 - Reduce the power consumption of the amplifier
- Settling response is obtained by
 - **Maximizing** the phase margin and
 - **Avoiding** pole-zero doublets in the passband of the amplifier
 - No pole-zero doublets in the passband for SMC
- Phase margin: 50 degree

$$PM = 180^\circ - \tan^{-1}\left(\frac{GBW}{p_1}\right) - \tan^{-1}\left(\frac{GBW}{p_2}\right) - \tan^{-1}\left(\frac{GBW}{p_3}\right) = 180^\circ - 90^\circ - \tan^{-1}\left(\frac{1}{2}\right) - \tan^{-1}\left(\frac{1}{4}\right)$$

- **Use a feedforward stage (a LHP zero) to increase the phase margin**

Single Miller Capacitor Feedforward Frequency Compensation Amplifier (SMFFC)

  - A feedforward path to provide an LHP zero to compensate the first nondominant pole
 - Adds current at the second-stage output
 - *Increases the output conductance of the stage*
 - Pushes the pole at the output of the second stage *to higher frequencies*



Small-signal Analysis of SMFFC

□ SMFFC

$$A_{v(SMFFC)} = \frac{A_{dc} \left(1 + s \frac{C_m g_{mf1}}{g_{m1} g_{m2}} - s^2 \frac{C_m C_{p2}}{g_{m2} g_{mL}} \right)}{\left(1 + \frac{s}{p_{-3dB}} \right) \left(1 + s \frac{C_L g_{o2}}{g_{m2} g_{mL}} + s^2 \frac{C_{p2} C_L}{g_{m2} g_{mL}} \right)}$$

LHP: low frequency
RHP: high frequency

z_{LHP} $+$ $-$ z_{LHP} z_{RHP}

where $A_{dc} = \frac{g_{m1} g_{m2} g_{mL}}{g_{o1} g_{o2} g_L}$, $p_{-3dB} = \frac{g_{o1} g_{o2} g_L}{g_{m2} g_{mL} C_m}$, $GBW = A_{dc} \cdot p_{-3dB} = \frac{g_{m1}}{C_m}$

Closed-loop with unity-gain feedback $A_{cl(SMFFC)}(s) \cong \frac{1 + s \frac{g_{mf1} C_m}{g_{m1} g_{m2}}}{1 + s \frac{g_{mf1} C_m}{g_{m1} g_{m2}} + \frac{s C_m}{g_{m1}} \left(1 + s \frac{C_L g_{o2}}{g_{m2} g_{mL}} + s^2 \frac{C_{p2} C_L}{g_{m2} g_{mL}} \right)}$

- Stability: by Routh-Hurwitz Criterion: $\frac{g_{o2}}{C_{p2}} > \frac{g_{m1}}{C_m} \left(\frac{1}{1 + g_{mf1}/g_{m2}} \right)$
- z_{LHP}, z_{RHP} : $z_{LHP} = \frac{g_{m1} g_{m2}}{g_{mf1} C_m}$, $z_{RHP} = \frac{g_{mf1} g_{mL}}{g_{m1} C_{p2}} + \frac{g_{m1} g_{m2}}{g_{mf1} C_m} \approx \frac{g_{mf1} g_{mL}}{g_{m1} C_{p2}}$

Small-signal analysis of SMFFC (cont'd)

- Phase margin: 75°



$$\begin{aligned} PM &= 180^\circ - \tan^{-1}\left(\frac{GBW}{p_1}\right) - \tan^{-1}\left(\frac{GBW}{p_2}\right) - \tan^{-1}\left(\frac{GBW}{p_3}\right) + \tan^{-1}\left(\frac{GBW}{z_{LHP}}\right) \\ &= 180^\circ - 90^\circ - \tan^{-1}\left(\frac{1}{2}\right) - \tan^{-1}\left(\frac{1}{4}\right) + \tan^{-1}\left(\frac{1}{2}\right) \end{aligned}$$

- **Exact pole-zero cancellation:**

$$p_2 = z_{LHP} = \frac{g_{m1}g_{m2}}{g_{mf1}C_m} \Rightarrow g_{mf1} = \frac{1}{A_{v2}} \frac{g_{m1}g_{m2}C_L}{g_{mL}C_m}$$


- The pole-zero doublet will **appear at high frequency** (around twice the bandwidth), the performance of the amplifier is not significantly disturbed
- C_m can **be further reduced** to achieve a still higher bandwidth **without sacrificing the stability of the amplifier**
 - Improve the slew rate of the amplifier

SMC

 
 


■ Schematic of the SMC amplifier


TRANSISTOR	SMC
Mb1	2*(5.55/1.05)
Mb2	8*(5.55/1.05)
M1,2	8*(6.15/0.6)
M3,4	6*(10.05/1.05)
M5,6	2*(10.05/1.05)
M7,8	6*(6.15/1.95)
M9	6*(6.3/0.6)
M10,11	2*(9/0.75)
M12	6*(5.55/0.6)
M14	10*(10.05/0.6)
M13	2*(9.3/0.6)
Mf1,2	-
Mb3	-

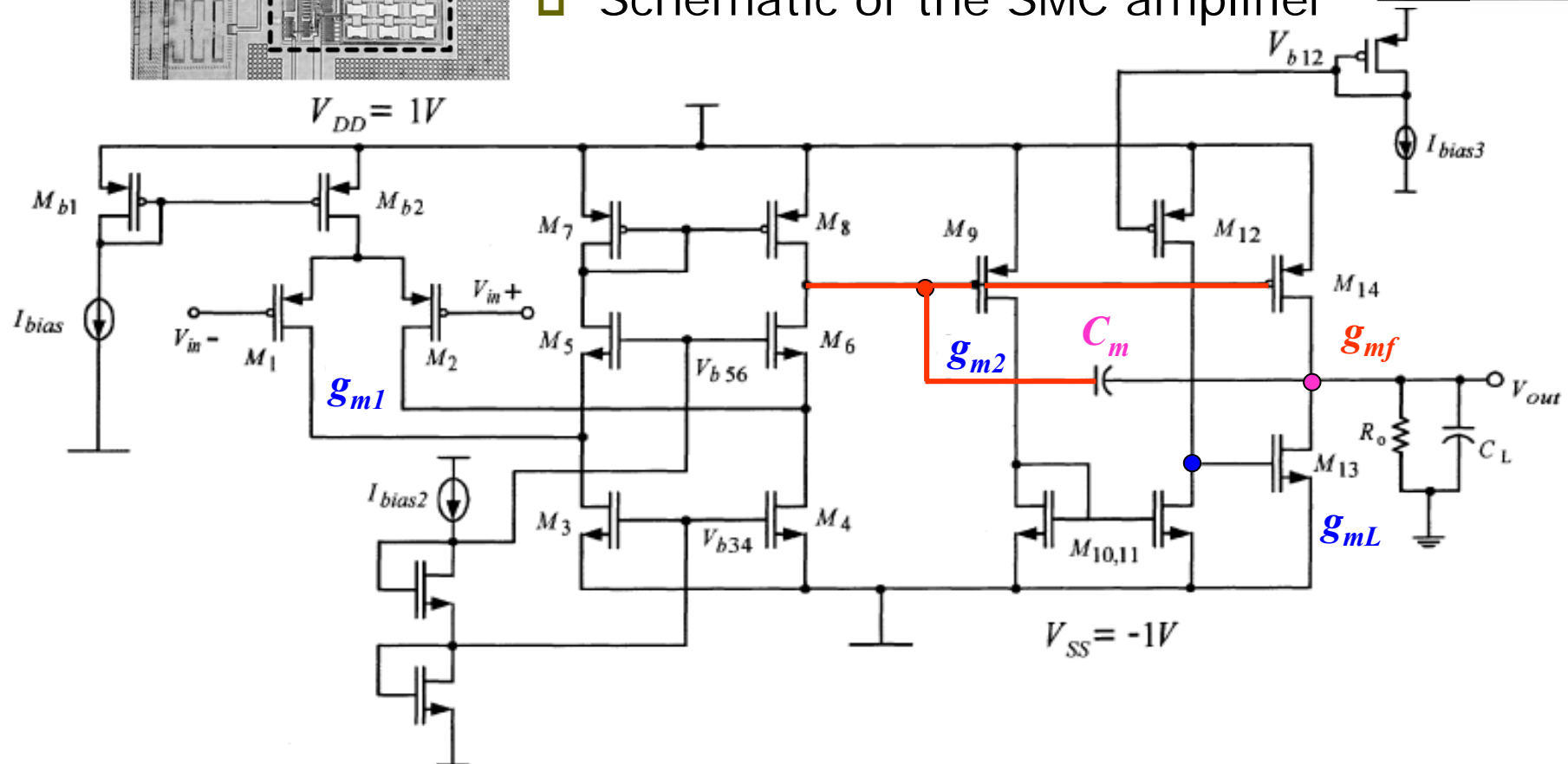

SMFFC

  


□ Schematic of SMFFC amplifier

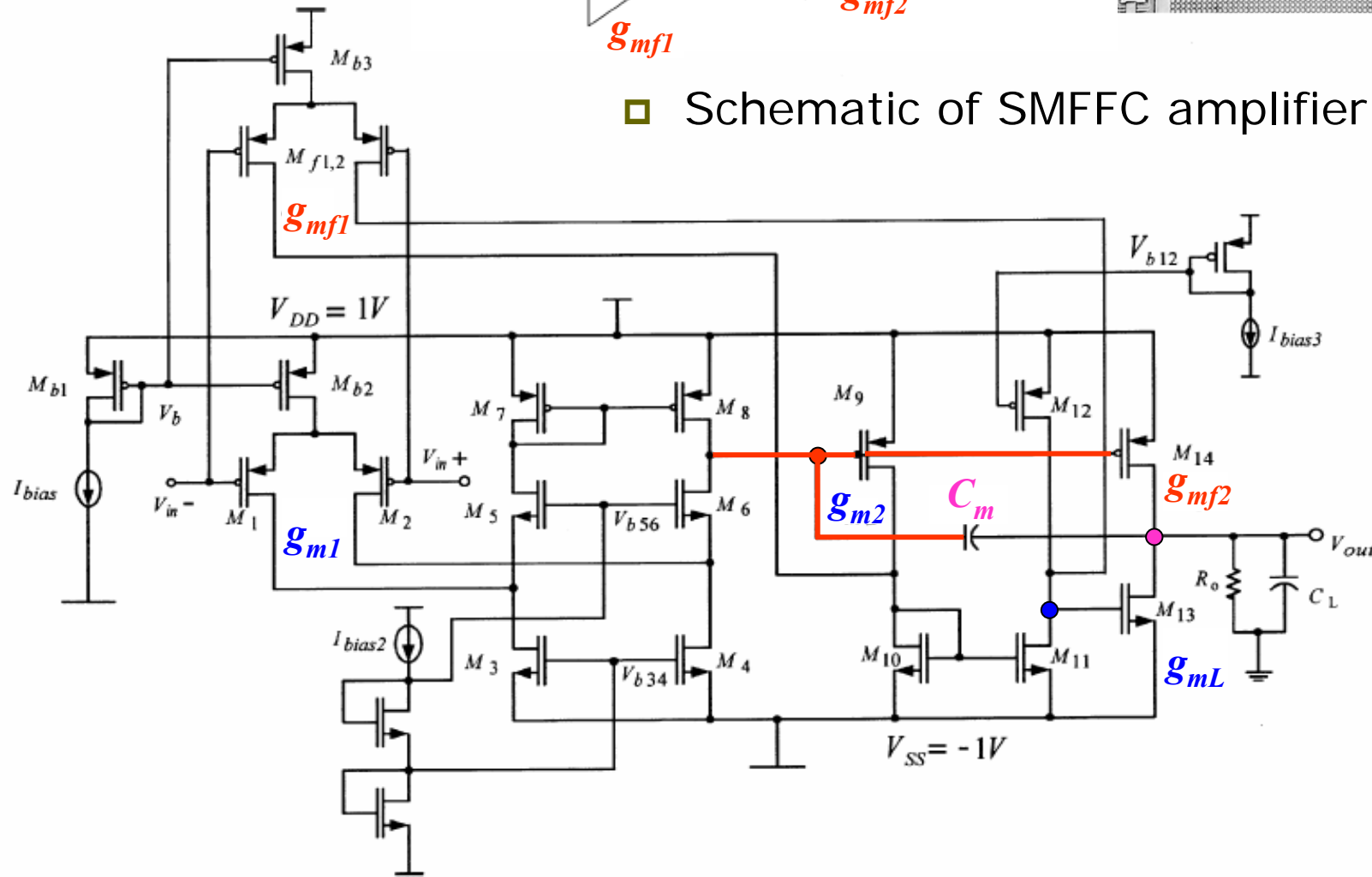

TRANSISTOR	SMFFC
Mb1	2*(5.55/1.05)
Mb2	8*(5.55/1.05)
M1,2	8*(6.15/0.6)
M3,4	6*(10.05/1.05)
M5,6	2*(10.05/1.05)
M7,8	6*(6.15/1.95)
M9	6*(6.3/0.6)
M10,11	2*(9/0.75)
M12	6*(5.55/0.6)
M14	10*(10.05/0.6)
M13	2*(9.3/0.6)
Mf1,2	6*(5.55/0.75)
Mb3	6*(5.55/1.05)

Experimental results (cont'd)

□ Transient response

 

- For the low voltage and the high voltage, the operating points of the transistors in the circuit are different, which means that the effective pole, zero locations of the amplifier are different for rising and falling signals
 - This is the reason why overshoot appears for up-going signal, and not for down-going signal

Comparison

COMPARISON OF DIFFERENT MULTISTAGE AMPLIFIERS WITH LARGE CAPACITIVE LOADS

PARAMETER	NMC [10]	DFCFC [8]	AFFC [10]	DLPC [11]	THIS WORK SMC	THIS WORK SMFFC
Load pF/K Ω	120/25	100/25	120/25	120/25	120/25	120/25
DC gain(dB)	>100	>100	>100	>100	>100	>100
GBW(MHz)	0.4	2.6	4.5	7	4.6	9
Phase margin	61°	43°	65°	46°	58°	57°
Power(mW@Vdd)	0.38 @2	0.42 @	0.4 @2	0.33@1.5	0.38@2	0.41@2
Capacitor Value (pF)	C _{m1} =88 C _{m2} =11	C _{m1} =18 C _{m2} =3	C _m =3 C _a =7	C _a =4.8 C _b =2.5	C _m =7 (one)	C _m =4 (one)
SR+(V/ μ S)	0.15	1.32	0.78	2.2	3.28	4.8
SR-(V/ μ S)	0.13	1.27	2.20	4.4	1.31	2
+1% TS (μ s)	4.9	0.96	0.42	0.315	0.53	0.58
-1% TS (μ s)	4.7	1.37	0.85	0.68	0.4	0.43
Area(mm ²)	0.140	0.110	0.060	0.050	0.020	0.015
Technology	0.8 μ m CMOS	0.8 μ m CMOS	0.8 μ m CMOS	0.6 μ m CMOS	0.5 μ m CMOS	0.5 μ m CMOS